
Unit 6. Sequential subsystems

Digital Electronic Circuits
E.T.S.I. Informática
Universidad de Sevilla

Jorge Juan-Chico <jjchico@dte.us.es> 2010-2021

This work is licensed under the Creative Commons Attribution-ShareAlike 4.0 International License. To view a copy of this license, visit <http://creativecommons.org/licenses/by-sa/4.0/> or send a letter to Creative Commons, PO Box 1866, Mountain View, CA 94042, USA.

Contents

- Introduction
- Registers
- Counters
- Design with sequential subsystems


Recommended readings and exercises

- Theory reference
 - LaMeres, 7.5: Counters from a FSM perspective.
- Verilog modeling reference
 - [verilog-course.v](#), unit 7.
 - LaMeres: 9.4, 9.5.
- Exercises from course's collection 6 (in Spanish)
 - Register design: 4, 19.
 - Counter design: 2, 10.
 - Counter design and count limit: 20
 - Sequence generator: 5a, 5b.
 - Counters based on other counters: 6.
 - Digital clock: 8.

Examples difficulty level



Easy

 

Moderate




Difficult

Introduction

- Sequential subsystem
 - Sequential circuit with n flip-flops that work together to do some task or set of tasks.
 - The operation is related to the n -bit data stored, not to individual bits.
 - The implemented functionality is general enough to find applications in multiple design problems.
- Basic types of sequential subsystems
 - Registers: store a n -bit word for its later use, with the possibility to apply transformation on the stored data.
 - Counters: specialized register that perform counting operations (increment, decrement, etc.) on the stored data.


Introduction

 

Introduction

- Control inputs
 - Select operation to perform.
 - Synchronous operations: take place with the active clock event.
 - Asynchronous operations: take place right after control signal activation.
 - Typical control signals:
 - CL: clear
 - EN: enable
 - LD: data load
- Data inputs: provide the data to be loaded
- Data outputs: give access to the store data
- State outputs: give information about the stored data or system state
 - Eg.: content is zero, count end, etc.

Modular design

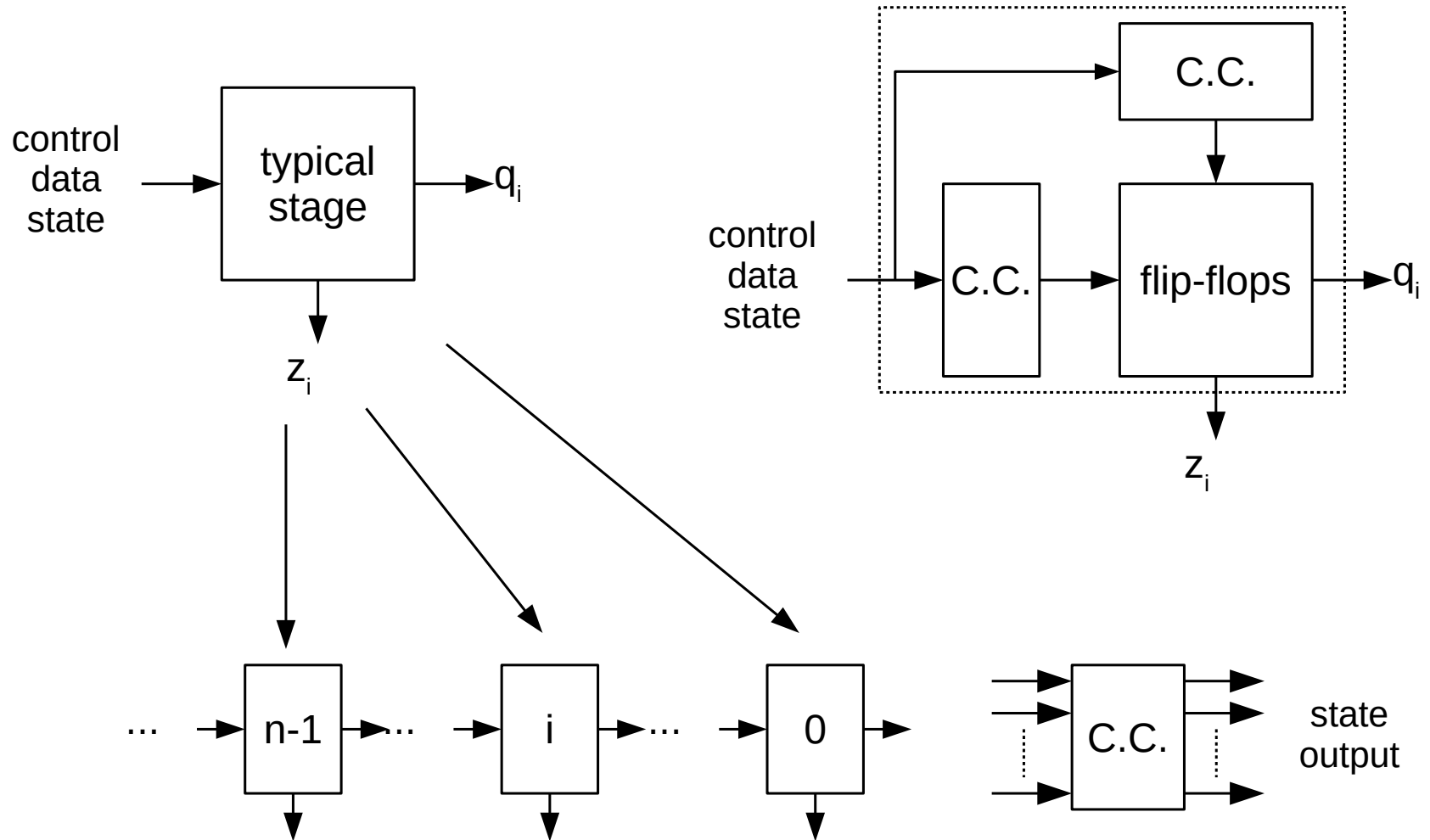

Modular design

- Modular structure
 - All the bits in the subsystem do a similar operation.
 - The operation and complexity of the system does not depend on the number of bits.
- Sequential subsystem design
 - Although a sequential subsystem can be described by a FSM it is not normally a good design methodology: big number of similar states.
 - Modular design approach:
 - Design a typical stage (1 bit).
 - Replicate the typical stage for the n bits in the system.
 - Include special cases: border bits and global signals.
 - The design complexity does not depend on the number of bits.

RT (Register Transfer) notation

- Used to represent multi-bit data assignment (like the contents of registers and counters).

| Type | Operators | Function | Examples | Verilog ex. |
|--------------------------|--|---|--|--|
| Sequential assignment | $A \leftarrow \langle \text{expr} \rangle$ | The value of $\langle \text{expr} \rangle$ is stored in register A. Storage takes place with the active clock edge. Registers in $\langle \text{expr} \rangle$ represent the current value. | $Q \leftarrow Q + A$ | <code>q <= q + a;</code> |
| Combinational assignment | $A = \langle \text{expr} \rangle$ | The value of A at each moment is obtained by evaluating $\langle \text{expr} \rangle$. | $A = B + C$ | <code>assign a = b + c;</code> |
| Arithmetic | $+, -, *, /, \dots$ | Arithmetic operations | $A = B * C$ $\text{CNT} \leftarrow \text{CNT} + 1$ | <code>a = b * c;</code> <code>cnt <= cnt + 1;</code> |
| Logic | $\&, , \wedge, \bar{}, \dots$ | Bitwise logic operations | $A = B \& \bar{C}$ | <code>a = b & ~c;</code> |
| Shift | $\text{SHL}(A,b)$ $\text{SHR}(A,b)$ | A is shifted one bit. The new bit is taken from 'b'. | $Q \leftarrow \text{SHL}(Q,0)$ $Z = \text{SHR}(X, X_R)$ | <code>q <= q << 1;</code> |
| Bit selection | $A[i], A_i$ | i-th bit in A is selected. | $Z = B_3$ | <code>z = b[3];</code> |
| Bit range selection | $A[i..j], A_{i..j}$ | Bits from i-th to j-th are selected. | $B = Q_{7..4}$ | <code>b = q[7:4];</code> |
| Chain | $\{A,B\}$ | The bits of two words are chained together to form a larger word. | $A \leftarrow \{B,C\}$ $D = \{A_{3..0}, B_{7..4}\}$ | <code>a <= {b,c};</code> <code>d = {a[3:0],b[7:4]};</code> |

Contents

- Introduction
- Registers
 - Register classification
 - Parallel-in, parallel-out register
 - Shift register
 - Universal register
- Counters
- Design with sequential subsystems

Registers

| | | | | | | | |
|---|---|---|---|---|---|---|---|
| 1 | 0 | 0 | 1 | 0 | 1 | 1 | 0 |
|---|---|---|---|---|---|---|---|


- n-bit storage element (n flip-flops)
 - Content is usually expressed by the data it represents and not by individual bits: number, character, etc.
 - Typically designed using D flip-flops: easier design.
 - All the flip-flops in the register share the same clock and asynchronous signals.
- Basic operations:
 - Write (load): stored data modification.
 - Read: access to the content of the register.

Registers. Classification


- Parallel input
 - All the bits can be written (loaded) at the same time (with the same clock event).
 - There is one load input signal for each stored bit.
- Serial input
 - Only one bit is loaded at each clock cycle.
 - A single input signal for all the stored bits (needs a bit shift operation).
- Parallel output
 - All the bits can be read at the same time.
 - One output signal for each stored bit.
- Serial output
 - Only one bit can be read at each clock cycle.
 - A single output signal for all the stored bits (needs a bit shift operation).

Registers. Classification


parallel-in/parallel-out

 


parallel-in/serial-out

 


serial-in/parallel-out

 

serial-in/serial-out

 

Parallel-in/parallel-out register

 


Verilog code

```
module reg(  
    input wire ck,  
    input wire cl,  
    input wire ld,  
    input wire [3:0] x,  
    output wire [3:0] z  
);  
  
    reg [3:0] q;  
  
    always @(posedge ck, negedge cl)  
        if (cl == 0)  
            q <= 0;  
        else if (ld == 1)  
            q <= x;  
  
    assign z = q;  
  
endmodule
```

Operation table

| CL, LD | Operation | Type |
|--------|------------------|--------|
| 0x | $q \leftarrow 0$ | async. |
| 11 | $q \leftarrow x$ | sync. |
| 10 | $q \leftarrow q$ | sync. |

Parallel-in/parallel-out register

 


Asynchronous operation table



| CL | Operation | Typ. stage | Excitation |
|----|------------------|----------------------|------------|
| 0 | $q \leftarrow 0$ | $q_i \leftarrow 0$ | $CL_i = 0$ |
| 1 | $q \leftarrow q$ | $q_i \leftarrow q_i$ | $CL_i = 1$ |

Synchronous operation table

| LD | Operation | Typ. stage | Excitation |
|----|------------------|----------------------|-------------|
| 1 | $q \leftarrow x$ | $q_i \leftarrow x_i$ | $D_i = x_i$ |
| 0 | $q \leftarrow q$ | $q_i \leftarrow q_i$ | $D_i = q_i$ |

 

Parallel-in/parallel-out register

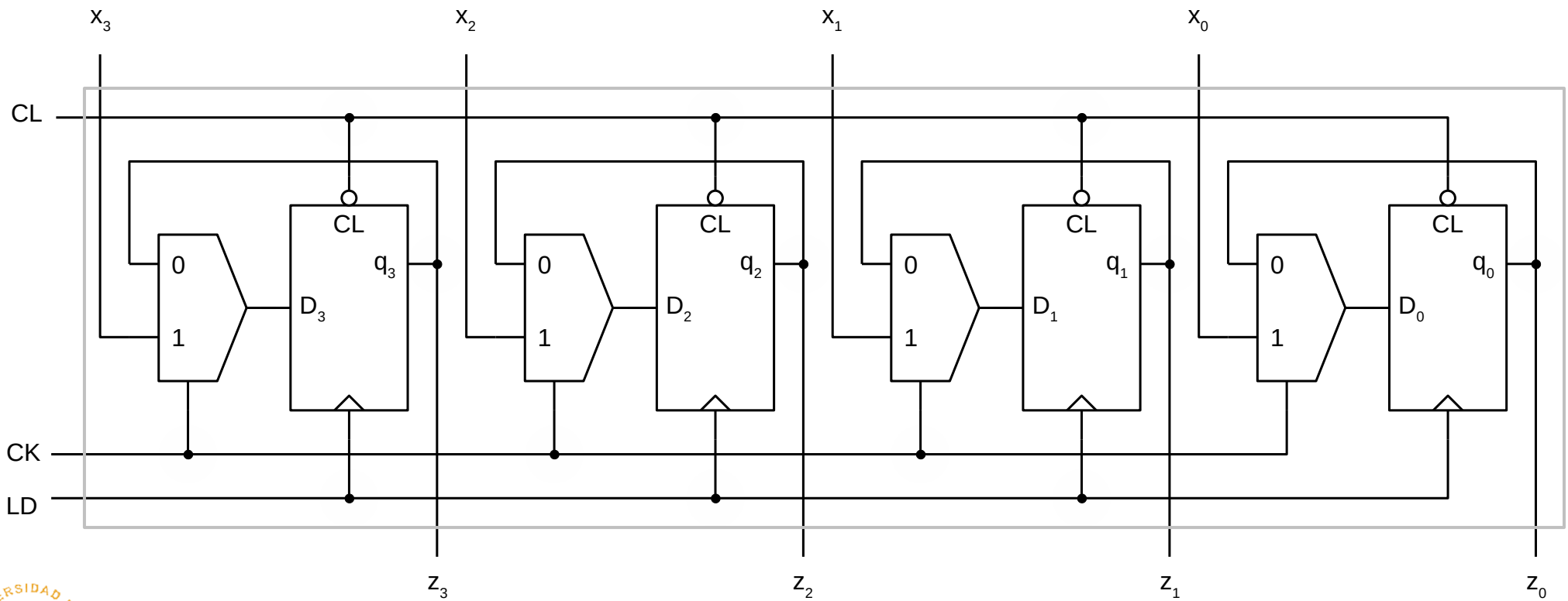 

Design alternatives




- The most straightforward method to design a register is using:
 - D flip-flops: input D is the next state.
 - Multiplexers: direct implementation of the operation table.
- But a register may be designed with any type of flip-flop and any type of combinational design technique.

Example 1

- a) Design a parallel-in/parallel-out register using D flip-flops and logic gates.
- b) Design a parallel-in/parallel-out register using JK flip-flops and multiplexers.
- c) Design a parallel-in/parallel-out register using JK flip-flops and logic gates.

Shift register

 


Operation table

| CL, EN | Operation | Type |
|--------|-----------------------------------|--------|
| 0x | $q \leftarrow 0$ | async. |
| 11 | $q \leftarrow \text{SHL}(q, x_L)$ | sync. |
| 10 | $q \leftarrow q$ | sync. |

Verilog code




```
module reg_shl(  
    input wire ck,  
    input wire cl,  
    input wire en,  
    input wire xl,  
    output wire zl  
);  
  
    reg [3:0] q;  
  
    always @(posedge ck, negedge cl)  
        if (cl == 0)  
            q <= 0;  
        else if (en == 1)  
            q <= {q[2:0], xl};  
  
    assign zl = q[3];  
  
endmodule
```

Shift register


 


Synchronous operation table

| EN | Operation | Typ. st. | St. 0 | Typ. ex. | St. 0 ex. |
|----|-----------------------------------|--------------------------|--|-----------------|-------------------------------|
| 1 | $q \leftarrow \text{SHL}(q, x_L)$ | $q_i \leftarrow q_{i-1}$ | $\mathbf{q}_0 \leftarrow \mathbf{x}_L$ | $D_i = q_{i-1}$ | $\mathbf{D}_0 = \mathbf{x}_L$ |
| 0 | $q \leftarrow q$ | $q_i \leftarrow q_i$ | $q_0 \leftarrow q_0$ | $D_i = q_i$ | $D_0 = q_0$ |

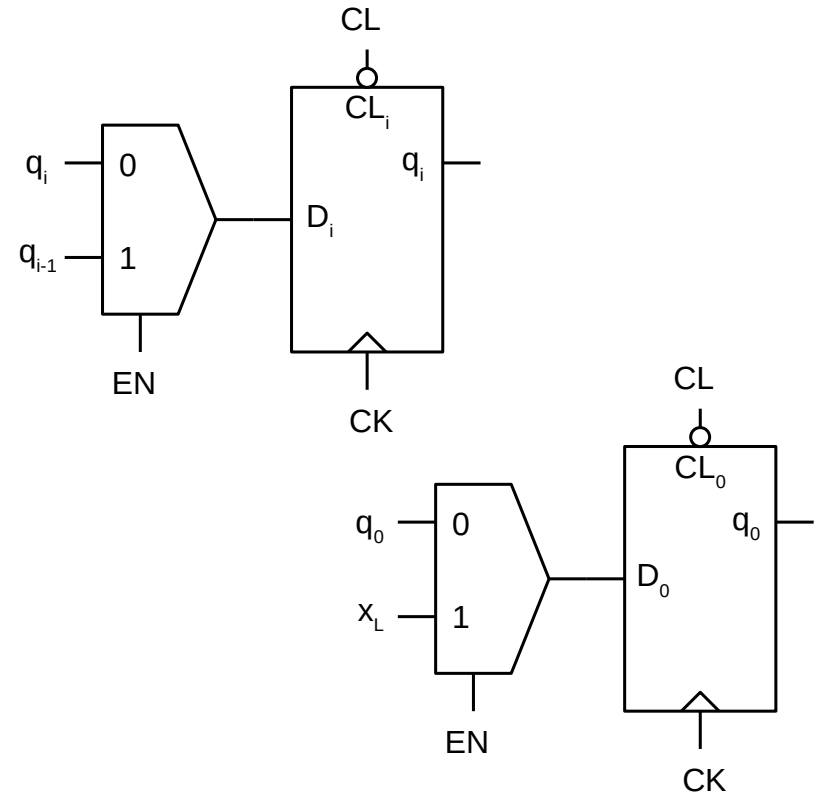 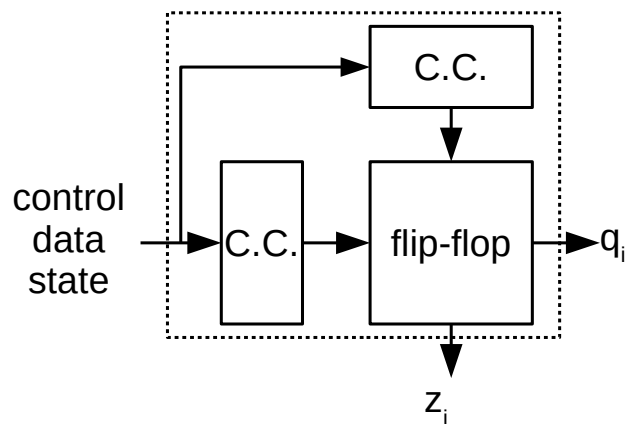


Shift register

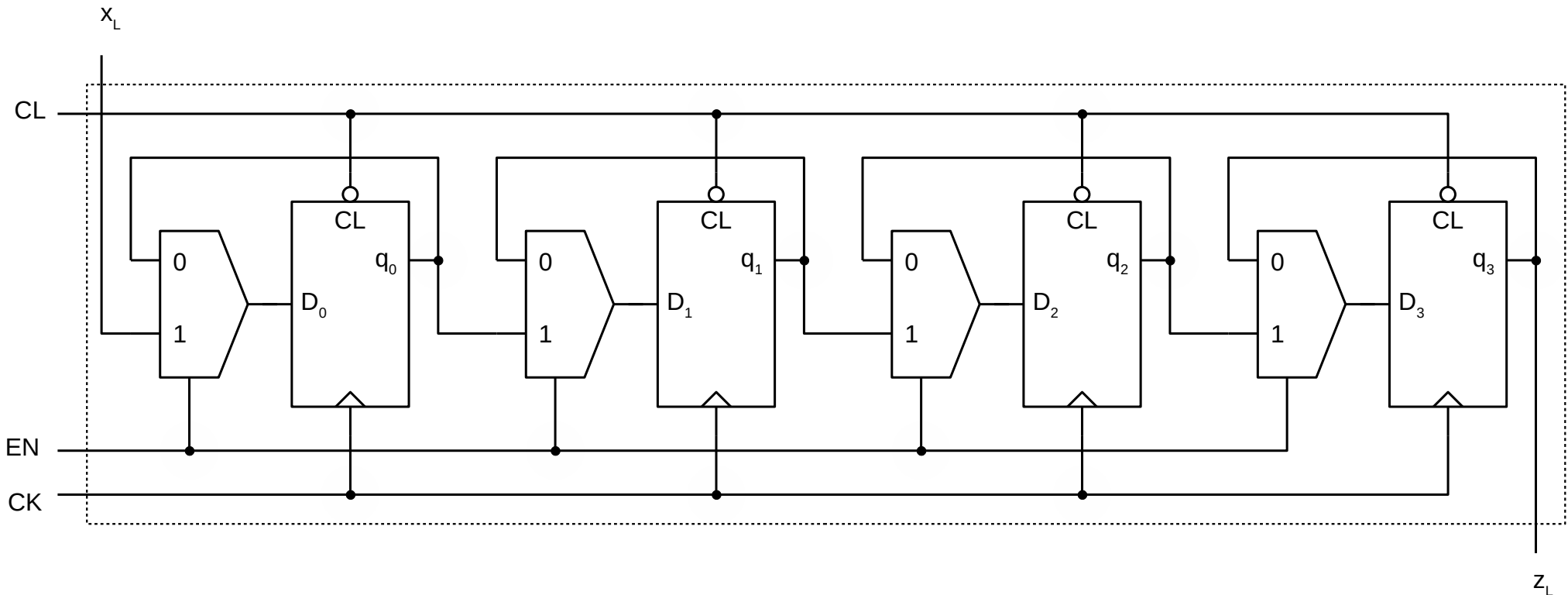 

Shift register

How to design a right-shift register?

Universal register

 

Verilog code

```

module ureg(
    input  wire  ck,
    input  wire  cl,
    input  wire  ld,
    input  wire  shr,
    input  wire  shl,
    input  wire [3:0] x,
    output wire [3:0] z
);

    reg [3:0] q;

    always @(posedge ck, negedge cl)
        if (cl == 0)
            q <= 0;
        else if (ld == 1)
            q <= x;
        else if (shr == 1)
            q <= {x[3], q[3:1]};
        else if (shl == 1)
            q <= {q[2:0], x[0]};

    assign z = q;


endmodule

```

Tabla de operación


| CL,LD,SHR,SHL | Operation | Type |
|---------------|-----------------------------------|--------|
| 0xxx | $q \leftarrow 0$ | async. |
| 11xx | $q \leftarrow x$ | sync. |
| 101x | $q \leftarrow \text{SHR}(q, x_R)$ | sync. |
| 1001 | $q \leftarrow \text{SHL}(q, x_L)$ | sync. |
| 1000 | $q \leftarrow q$ | sync. |

Universal register

 


| LD,SHR,SHL | Operation | Typ. stage | St. n-1 | St. 0 | Typ. exc. | Exc. n-1 | Exc. 0 |
|------------|-----------------------------------|--------------------------|------------------------------|----------------------|-----------------|---------------------|-------------|
| 1xx | $q \leftarrow x$ | $q_i \leftarrow x_i$ | $q_{n-1} \leftarrow x_{n-1}$ | $q_0 \leftarrow x_0$ | $D_i = x_i$ | $D_{n-1} = x_{n-1}$ | $D_0 = x_0$ |
| 01x | $q \leftarrow \text{SHR}(q, x_R)$ | $q_i \leftarrow q_{i+1}$ | $q_{n-1} \leftarrow x_R$ | $q_0 \leftarrow q_1$ | $D_i = q_{i+1}$ | $D_{n-1} = x_R$ | $D_0 = q_1$ |
| 001 | $q \leftarrow \text{SHL}(q, x_L)$ | $q_i \leftarrow q_{i-1}$ | $q_{n-1} \leftarrow q_{n-2}$ | $q_0 \leftarrow x_L$ | $D_i = q_{i-1}$ | $D_{n-1} = q_{n-2}$ | $D_0 = x_L$ |
| 000 | $q \leftarrow q$ | $q_i \leftarrow q_i$ | $q_{n-1} \leftarrow q_{n-1}$ | $q_0 \leftarrow q_0$ | $D_i = q_i$ | $D_{n-1} = q_{n-1}$ | $D_0 = q_0$ |

Universal register

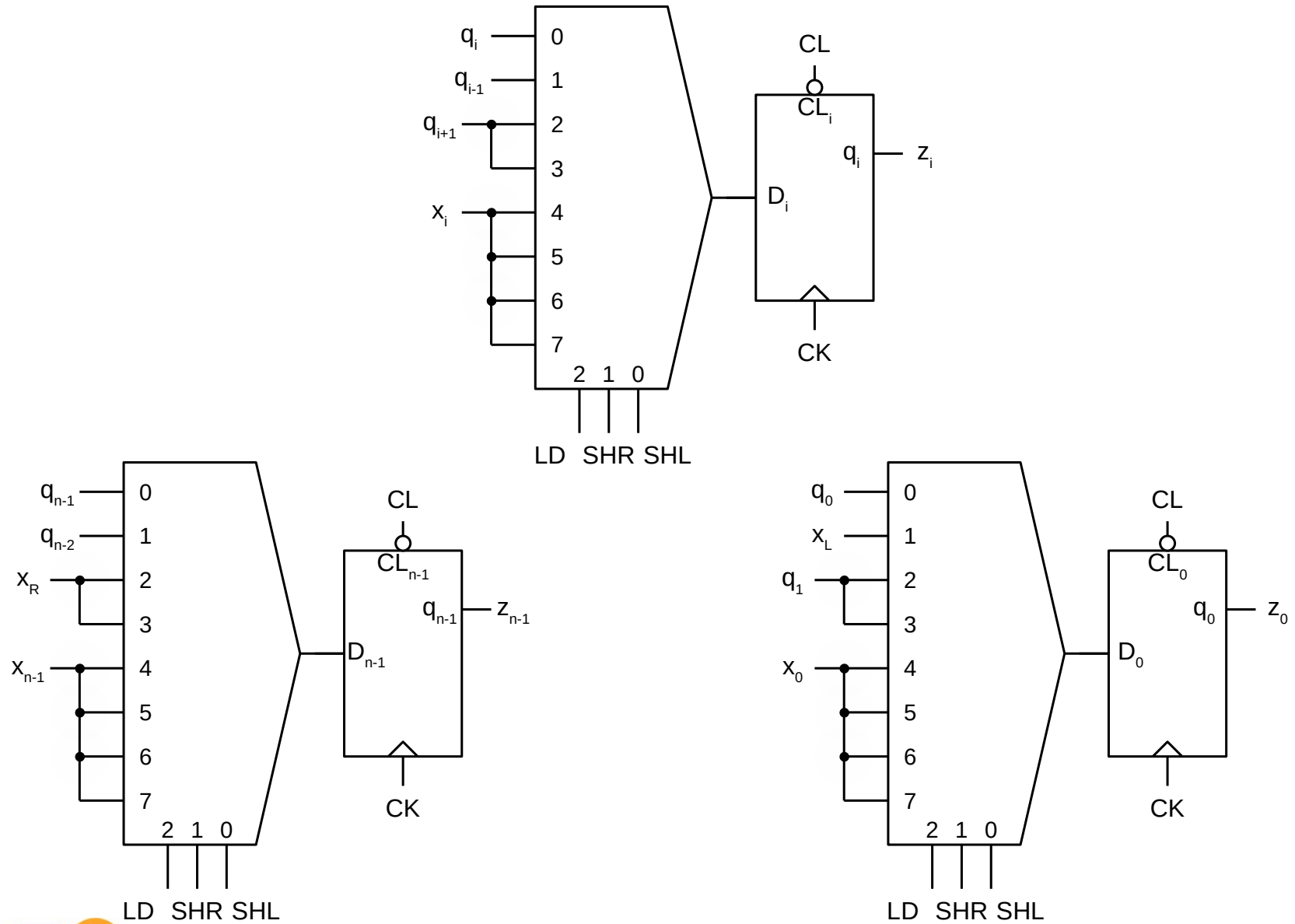

Universal register

Alternative implementation

 

Excitation equations (“receipts”) for register design using D flip-flops

| Description | Operation | Stages | Excitations |
|--------------------|-----------------------------------|--|------------------------------------|
| Inhibition | $q \leftarrow q$ | $q_i \leftarrow q_i$ | $D_i = q_i$ |
| Parallel load | $q \leftarrow x$ | $q_i \leftarrow x_i$ | $D_i = x_i$ |
| Left shift | $q \leftarrow \text{SHL}(x, x_L)$ | $q_i \leftarrow q_{i-1}$ $q_0 \leftarrow x_L$ | $D_i = q_{i-1}$ $D_0 = x_L$ |
| Right shift | $q \leftarrow \text{SHR}(x, x_R)$ | $q_i \leftarrow q_{i+1}$ $q_{n-1} \leftarrow x_R$ | $D_i = q_{i+1}$ $D_{n-1} = x_R$ |
| Synchronous clear | $q \leftarrow 0$ | $q_i \leftarrow 0$ | $D_i = 0$ |
| Asynchronous clear | $q \leftarrow 0$ | $q_i \leftarrow 0$ | $CL_i = 1$ |




Example

 Example 2

Design the register specified below using D flip-flops.

Note: the clear input (CL) is synchronous.



| CL,LD,SHR | Operación |
|-----------|-----------------------------------|
| 1xx | $q \leftarrow 0$ |
| 01x | $q \leftarrow x$ |
| 001 | $q \leftarrow \text{SHR}(q, x_R)$ |
| 000 | $q \leftarrow q$ |

Contents

- Introduction
- Registers
- Counters
 - Binary up counter modulus 2^n
 - Count limiting
 - Down counter
 - Up/down counter
 - Non-binary counters
- Design with sequential subsystems


Counters

- Similar to the register: adds count operation
- Design
 - Same modular design principles.
 - Easier implementation with T or JK flip-flops (simplified count operation).
- Typical operations
 - Up counting.
 - Down counting.
 - Reset (clear).
 - Count state loading.
- Typical output
 - Count state: current value of the count.
 - End-of-count (EOC): counter in the last count value.

Binary modulus 2^n up counter

- Modulus
 - Number of counter's states.
- Binary
 - Count states are consecutive base-2 numbers.
- Modulus 2^n
 - Counts from 0 to 2^n-1 (n bits).
- Up
 - Count increases: 0, 1, 2, 3, ...
- Cyclic count
 - First count state follows last count state (overflow).
 - Eg. 4-bit counter: ... 13, 14, 15, 0, 1, 2, ...

Binary modulus 2^n up counter

 

Operation table


| CL | Operation | Type |
|----|--------------------------------|--------|
| 1 | $q \leftarrow 0$ | async. |
| 0 | $q \leftarrow (q+1) \bmod 2^n$ | sync. |

Verilog code

```
module count_mod16(  
    input wire ck,  
    input wire cl,  
    output wire [3:0] z  
);  
  
    reg [3:0] q;  
  
    always @(posedge ck, posedge cl)  
        if (cl == 1)  
            q <= 0;  
        else  
            q <= q + 1;  
  
    assign z = q;  
  
endmodule
```


Binary modulus 2^n up counter

Count operation

 

| | | | | | |
|---|----|----|----|----|----|
| | JK | 00 | 01 | 11 | 10 |
| q | 0 | 0 | 0 | 1 | 1 |
| | 1 | 1 | 0 | 0 | 1 |

$q \leftarrow$

$$q_i = \begin{cases} \bar{q}_i, & \text{if } q_j = 1 \forall j < i \\ q_i, & \text{in other case} \end{cases}$$

$$q_i = \begin{cases} \bar{q}_i, & \text{si } q_{i-1} q_{i-2} \dots q_0 = 1 \\ q_i, & \text{si } q_{i-1} q_{i-2} \dots q_0 = 0 \end{cases}$$

$$q_i = \begin{cases} \bar{q}_i, & \text{if } J_i = K_i = 1 \\ q_i, & \text{if } J_i = K_i = 0 \end{cases}$$


$$q_j = 1 \forall j < i \Leftrightarrow q_{i-1} q_{i-2} \dots q_0 = 1$$

$$J_i = K_i = q_{i-1} \dots q_0$$

| Operation | Typical stage | Stage 1 | Stage 0 |
|--------------------------------|---|---|----------------------------|
| $q \leftarrow (q+1) \bmod 2^n$ | $q_i \leftarrow \bar{q}_i$ si $q_{i-1} \dots q_0 = 1$, q_i si $q_{i-1} \dots q_0 = 0$ | $q_1 \leftarrow \bar{q}_1$ si $q_0 = 1$, q_1 si $q_0 = 0$ | $q_0 \leftarrow \bar{q}_0$ |




| Operation | Typ. stage excitation | St.1 excitation | St. 0 excitation |
|--------------------------------|---------------------------------|-------------------|------------------|
| $q \leftarrow (q+1) \bmod 2^n$ | $J_i = K_i = q_{i-1} \dots q_0$ | $J_1 = K_1 = q_0$ | $J_0 = K_0 = 1$ |

Binary modulus 2^n up counter

 

Synchronous operation table

| Operation | Typ. st. excitation | St. 1 exc. | St. 0 exc. |
|--------------------------------|-----------------------------|---------------|-------------|
| $q \leftarrow (q+1) \bmod 2^n$ | $J_i=K_i=q_{i-1} \dots q_0$ | $J_1=K_1=q_0$ | $J_0=K_0=1$ |

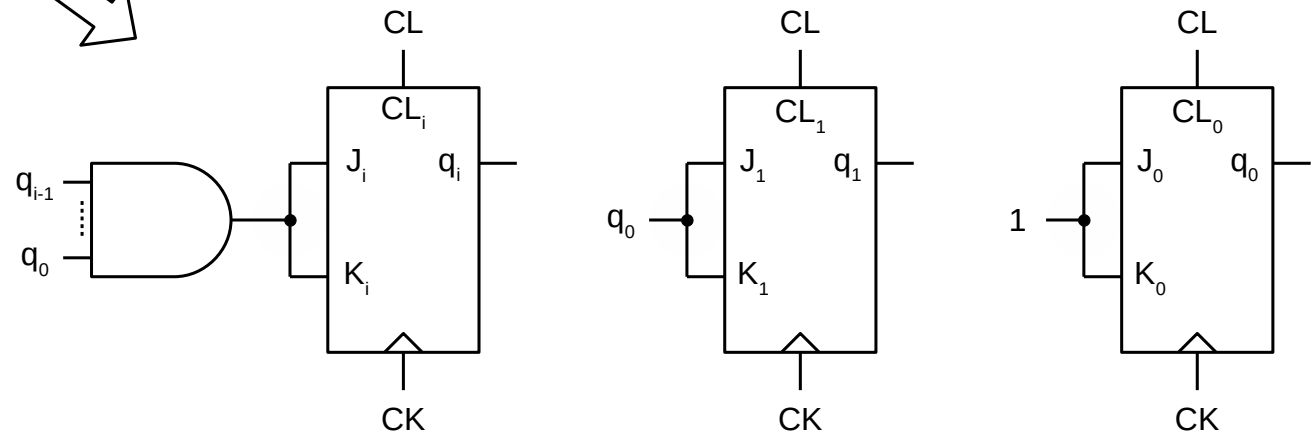 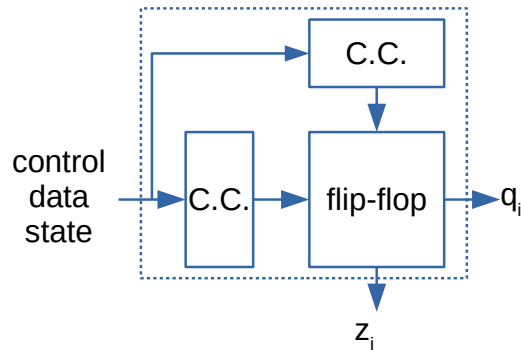

Design alternatives



- JK flip-flops are convenient to design counter by hand because:
 - It is easy to implement the counting operation: $J_i = K_i = q_0 \dots q_{i-1}$
 - It is easy to implement other operations as well.
- As with registers, counters can actually be implemented using any type of flip-flop.

Example 3

- a) Design a binary modulus 2^n up counter using T flip-flops.
- b) Design a binary modulus 2^n up counter using D flip-flops.

FPGA's building blocks only typically include D flip-flops, so all counters, registers and sequential logic in general are implemented using only D flip-flops in the end.

Binary modulus 2^n up counter with “clear” and “enable” inputs

 



Tabla de operación

| CL, EN | Operation | Type |
|--------|--------------------------------|-------|
| 1x | $q \leftarrow 0$ | sync. |
| 01 | $q \leftarrow (q+1) \bmod 2^n$ | sync. |
| 00 | $q \leftarrow q$ | sync. |

Verilog code

```
module count_mod16(  
    input wire ck,  
    input wire cl,  
    input wire en,  
    output wire [3:0] z  
);  
  
    reg [3:0] q;  
  
    always @(posedge ck)  
        if (cl == 1)  
            q <= 0;  
        else if (en == 1)  
            q <= q + 1;  
  
    assign z = q;  
  
endmodule
```

 Binary modulus 2^n up counter with “clear” and “enable” inputs



| | | | | | |
|---|----|-----|----|----|----|
| | JK | 00 | 01 | 11 | 10 |
| q | 0 | 0 | 0 | 1 | 1 |
| | 1 | 1 | 0 | 0 | 1 |
| | | q ← | | | |

| Description | Operation | Stage | St. excitation |
|-------------------|------------------|----------------------|----------------|
| Inhibition | $q \leftarrow q$ | $q_i \leftarrow q_i$ | $J_i=K_i=0$ |
| Synchronous clear | $q \leftarrow 0$ | $q_i \leftarrow 0$ | $J_i=0, K_i=1$ |

Binary modulus 2^n up counter with “clear” and “enable” inputs


 


Tabla de operación síncrona


| CL,EN | Operation | Typ. stage | Stage 1 | Stage 0 |
|-------|--------------------------------|-----------------------------|---------------------------------|-------------------------------|
| 1x | $q \leftarrow 0$ | $J_i=0, K_i=1$ | $J_1=0, K_1=1$ | $J_0=0, K_0=1$ |
| 01 | $q \leftarrow (q+1) \bmod 2^n$ | $J_i=K_i=q_{i-1} \dots q_0$ | $J_1=K_1=q_0$ | $J_0=K_0=1$ |
| 00 | $q \leftarrow q$ | $J_i=K_i=0$ | $J_1=K_1=0$ | $J_0=K_0=0$ |

MUX 4:1 implementation

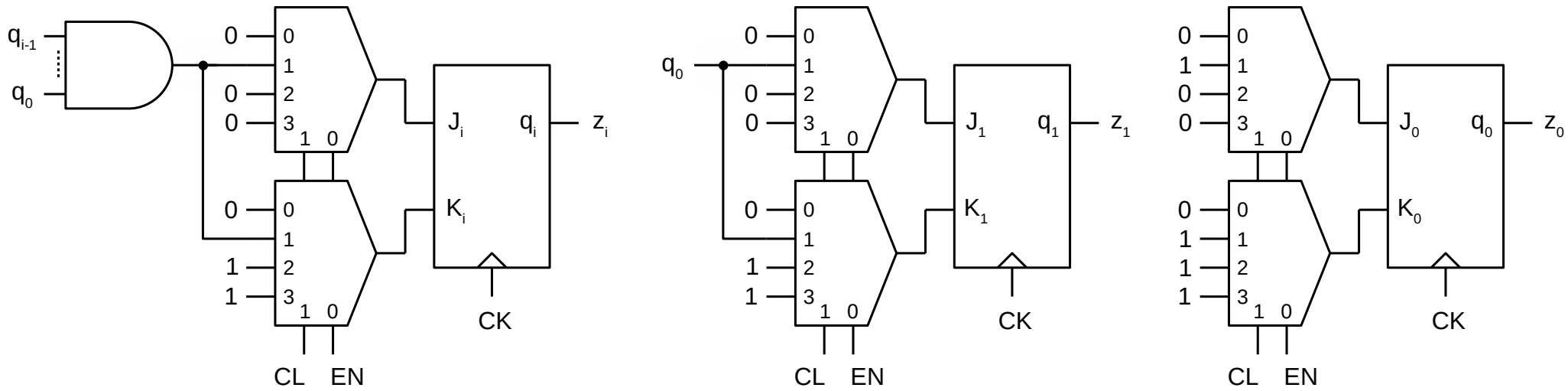

Binary modulus 2^n up counter with “clear” and “enable” inputs


Alternative implementations

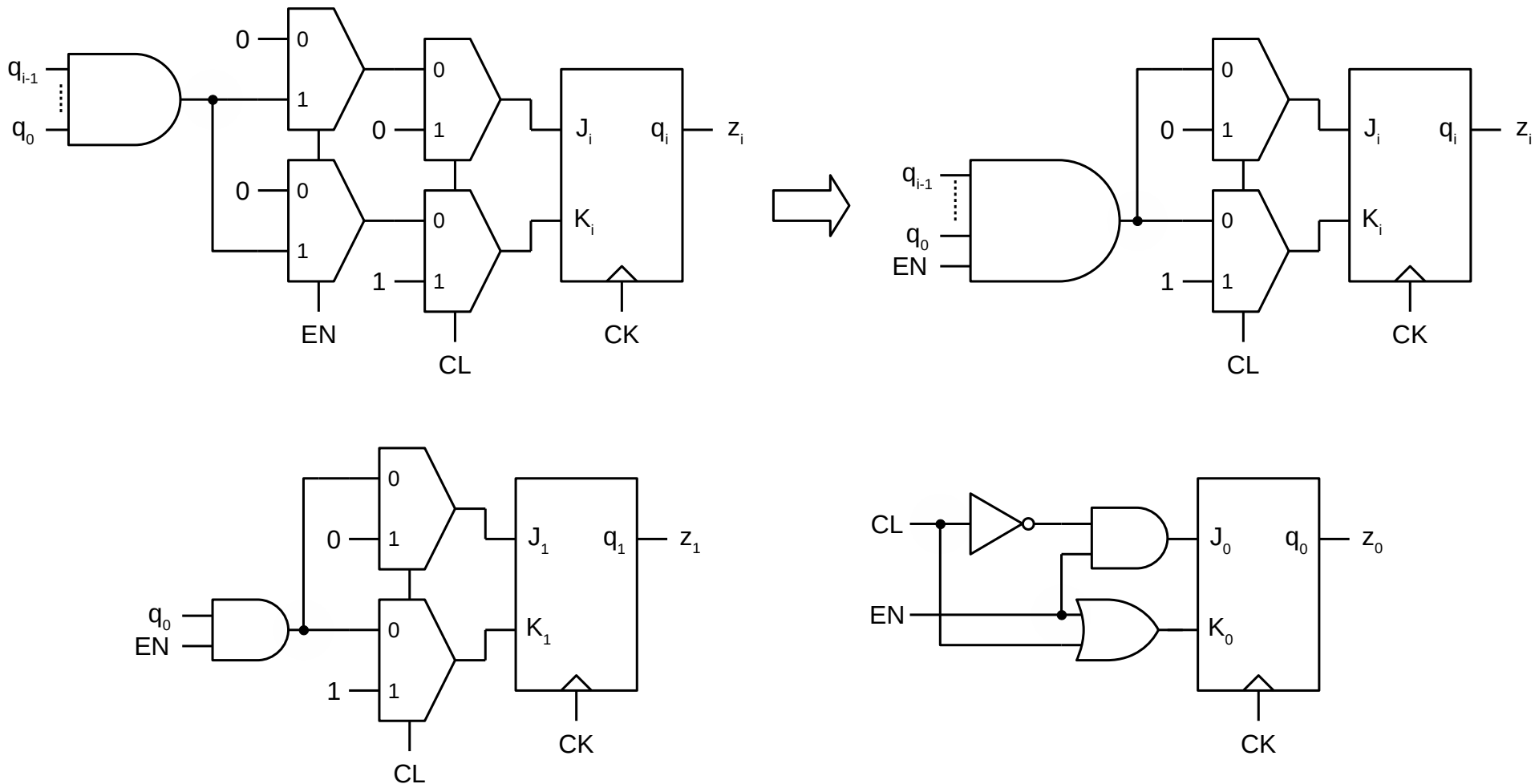


End-of-count output

- Up counter end-of-count (carry)
 - $C = 1$ if and only if $q = 2^n - 1$

$$C = q_{n-1} q_{n-2} \cdots q_0$$

 

End-of-count output

 

Verilog code

```
module count_mod16(  
    input wire ck,  
    input wire cl,  
    input wire en,  
    output wire [3:0] z,  
    output wire c  
);  
  
    reg [3:0] q;  
  
    always @(posedge ck)  
        if (cl == 1)  
            q <= 0;  
        else if (en == 1)  
            q <= q + 1;  
  
    assign z = q;  
    assign c = &q;  
  
endmodule
```

Counter combination

- Objective: combine two or more counters to obtain a bigger (more states) counter.
 - Module-k + module-l → Module-k*l
- Design:
 - Increment the most significant counter only when the least significant counter reaches its last state.
 - Counter combination is easier with appropriate inputs and outputs:
 - End-of-count: detect when a counter is at the maximum value.
 - Enable: enable a counter easily.

Example


Example 4

We have modulus-16 counters with synchronous clear (CL) and enable (EN) inputs, and end-of-count (carry) output (C). Using these counters and some logic gates we want to build:

 - a) A modulus-256 counter with a synchronous clear input (CL).
- b) A modulus-256 counter with a synchronous clear (CL) and enable (EN) inputs and end-of-count (carry) output (C).

Clue: you do not need any gates to build counter (a), but you do for counter (b).

Binary modulus 2^n up counter with “load” and “enable” inputs




Verilog code

```
module count_mod16(  
    input wire ck,  
    input wire ld,  
    input wire en,  
    input wire [3:0] x,  
    output wire [3:0] z  
);  
  
    reg [3:0] q;  
  
    always @(posedge ck)  
        if (ld == 1)  
            q <= x;  
        else if (en == 1)  
            q <= q + 1;  
  
    assign z = q;  
  
endmodule
```

Operation table

| LD, EN | Operation | Type |
|--------|--------------------------------|-------|
| 1x | $q \leftarrow x$ | sync. |
| 01 | $q \leftarrow (q+1) \bmod 2^n$ | sync. |
| 00 | $q \leftarrow q$ | sync. |

 
Binary modulus 2^n up counter with “load” and “enable” inputs



| | | | | | |
|---|---|-----|----|----|----|
| | | JK | | | |
| | | 00 | 01 | 11 | 10 |
| q | 0 | 0 | 0 | 1 | 1 |
| | 1 | 1 | 0 | 0 | 1 |
| | | q ← | | | |

| Description | Operation | Stage | St. excitation | St. excitation |
|-------------------|------------------|----------------------|--|---------------------------------------|
| Carga en paralelo | $q \leftarrow x$ | $q_i \leftarrow x_i$ | $J_i=1, K_i=0$ if $x=1$ $J_i=0, K_i=1$ if $x=0$ | $J_i = x_i$ $K_i = \overline{x_i}$ |

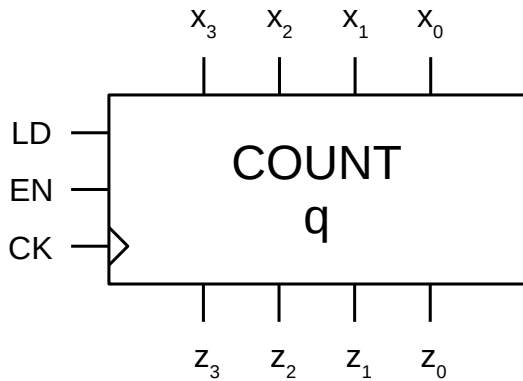Binary modulus 2^n up counter with "load" and "enable" inputs



| LD,EN | Operation | Typ. stage | Stage 1 | Stage 0 |
|-------|-------------------------------|---------------------------------|-------------------------------------|-----------------------------------|
| 1x | $q \leftarrow x$ | $J_i = x_i, K_i = \bar{x}_i$ | $J_1 = x_1, K_1 = \bar{x}_1$ | $J_0 = x_0, K_0 = \bar{x}_0$ |
| 01 | $q \leftarrow (q+1) \bmod 16$ | $J_i = K_i = q_{i-1} \dots q_0$ | $J_1 = K_1 = q_0$ | $J_0 = K_0 = 1$ |
| 00 | $q \leftarrow q$ | $J_i = K_i = 0$ | $J_1 = K_1 = 0$ | $J_0 = K_0 = 0$ |

