
Digital Circuits I

DAPA
E.T.S.I. Informática
Universidad de Sevilla
10/2012

Jorge Juan <jjchico@dte.us.es> 2010, 2011, 2012

You are free to copy, distribute and communicate this work publicly and make derivative work provided you cite the source and respect the conditions of the Attribution-Share alike license from Creative Commons.

You can read the complete license at:

<http://creativecommons.org/licenses/by-sa/3.0>



Departamento de Tecnología Electrónica - Universidad de Sevilla


Contents

- Logic functions
 - Logic operators
 - Logic expressions
 - Canonical forms
 - Design approach
- Boolean algebra
- Expression minimization
- Don't cares
- Functional analysis
- Timing analysis



Departamento de Tecnología Electrónica - Universidad de Sevilla

Logic functions

 

Formal specification
(truth table)


a	b	c	z
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

Verbal specification

Output a "1" if two or more inputs are equal to "1". Output "0" otherwise.

- Truth table: formal specification. Output value for every input combination (n inputs: 2^n input values).
- Combinational (digital) circuits implement logic functions.

Two-input logic functions

 

x y	F ₀	F ₁	F ₂	F ₃	F ₄	F ₅	F ₆	F ₇	F ₈	F ₉	F ₁₀	F ₁₁	F ₁₂	F ₁₃	F ₁₄	F ₁₅
00	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1
01	0	0	0	0	1	1	1	1	0	0	0	0	1	1	1	1
10	0	0	1	1	0	0	1	1	0	0	1	1	0	0	1	1
11	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1
		AND					XOR	OR	NOR	XNOR					NAND	


In general, there are $2^{(2^n)}$ functions of n variables

Logic operators and corresponding gates

NOT

x	z
0	1
1	0


$$z = \bar{x}$$

 

AND

x y	z
0 0	0
0 1	0
1 0	0
1 1	1


$$z = x \cdot y$$

 

OR

x y	z
0 0	0
0 1	1
1 0	1
1 1	1

$$z = x + y$$

 

Logic operators and corresponding gates

NAND

x y	z
0 0	1
0 1	1
1 0	1
1 1	0


$$z = \overline{x \cdot y}$$



NOR

x y	z
0 0	1
0 1	0
1 0	0
1 1	0


$$z = \overline{x + y}$$

 

XOR

x y	z
0 0	0
0 1	1
1 0	1
1 1	0


$$z = x \oplus y = \bar{x}y + x\bar{y}$$

 


XNOR

x y	z
0 0	1
0 1	0
1 0	0
1 1	1
 
$$z = \overline{x \oplus y} = \bar{x}\bar{y} + xy$$



Logic expressions

 


An expression for a function can always be obtained by combining the NOT, AND and OR operators.
Method:

1. For every "1" of the function, build a product term that is "1" for that input combination only.
2. Sum (OR) all the terms.


The resulting expression is a sum-of-products (S-O-P)
Terms containing all the literals are "**minterms**".
The sum-of-minterms is known as "**canonical form of minterms**"

a	b	c	z
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1
 
$$z = \bar{a}bc + a\bar{b}c + ab\bar{c} + abc$$



Logic expressions

 


An expression for a function can always be obtained by combining the NOT, AND and OR operators.
Method:

1. For every "0" of the function, build a sum term that is "0" for that input combination only.
2. Multiply (AND) all the terms.

The resulting expression is a product-of-sums (P-O-S)
Terms containing all the literals are "**maxterms**".
The sum-of-maxterms is known as "**canonical form of maxterms**"

a	b	c	z
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1
 
$$z = (a+b+c) \cdot (a+b+\bar{c}) \cdot (a+\bar{b}+c) \cdot (\bar{a}+b+c)$$



Canonical form notation

a b c	minterms	m-notat.
0 0 0	$\bar{a} \bar{b} \bar{c}$	m0
0 0 1	$\bar{a} \bar{b} c$	m1
0 1 0	$\bar{a} b \bar{c}$	m2
0 1 1	$\bar{a} b c$	m3
1 0 0	$a \bar{b} \bar{c}$	m4
1 0 1	$a \bar{b} c$	m5
1 1 0	$a b \bar{c}$	m6
1 1 1	$a b c$	m7

$$z = \bar{a}bc + a\bar{b}c + ab\bar{c} + abc$$

$$z = m3 + m5 + m6 + m7$$

$$z = \Sigma(3,5,6,7)$$

minterm: input combination for which the function is "1"

a b c	maxterm	M-notation
0 0 0	$a+b+c$	M0
0 0 1	$a+b+\bar{c}$	M1
0 1 0	$a+\bar{b}+c$	M2
0 1 1	$a+\bar{b}+\bar{c}$	M3
1 0 0	$\bar{a}+b+c$	M4
1 0 1	$\bar{a}+b+\bar{c}$	M5
1 1 0	$\bar{a}+\bar{b}+c$	M6
1 1 1	$\bar{a}+\bar{b}+\bar{c}$	M7

$$z = (a+b+c)(a+b+\bar{c})(a+\bar{b}+c)(\bar{a}+b+c)$$


$$z = M0 M1 M2 M4$$

$$z = \Pi(0,1,2,4)$$

maxterm: input combination for which the function is "0"

Logic design approach
 
$$z = \bar{a}bc + a\bar{b}c + ab\bar{c} + abc$$



S-O-P can be directly mapped to a digital circuits using three basic gates:

- Inverters (complements)
- AND (products)
- OR (sum)


¿Is the result minimum?

Contents

- Logic functions
- **Boolean algebra**
- **Expression minimization**
- Don't cares
- Functional analysis
- Timing analysis

Boolean algebra

 - {NOT, AND, OR} operators are a "Boolean algebra"



George Boole (1815-1864)

Elementary	$x+0 = x$ $x+1 = 1$ $x+x = x$ $x+\bar{x} = 1$ $\overline{(\bar{x})} = x$	$x \cdot 1 = x$ $x \cdot 0 = 0$ $x \cdot x = x$ $x \cdot \bar{x} = 0$
Commutativity	$x+y = y+x$	$x \cdot y = y \cdot x$
Associativity	$(x+y)+z = x+(y+z)$	$(x \cdot y) \cdot z = x \cdot (y \cdot z)$
Distributivity	$x \cdot (y+z) = (x \cdot y) + (x \cdot z)$	$x + (y \cdot z) = (x+y) \cdot (x+z)$
Reduction	$(x \cdot y) + (x \cdot \bar{y}) = x$	$(x+y) \cdot (x+\bar{y}) = x$
De Morgan's	$\overline{(x+y+\dots)} = \bar{x} \cdot \bar{y} \cdot \dots$	$\overline{(x \cdot y \cdot \dots)} = \bar{x} + \bar{y} + \dots$

Duality: if an expression holds, the expression that results from interchanging + with \cdot and 0 with 1 also holds.

Boolean algebra

- Precedence of \cdot over $+$
 - $x+(y \cdot z) = x+y \cdot z$
- "." can be omitted
 - $x+y \cdot z = x+yz$

Minimization

$$xy + x\bar{y} = x$$

"x" can be any expression

$$\begin{array}{l} z = \bar{a}bc + a\bar{b}c + ab\bar{c} + abc \longrightarrow \text{0-term} \\ \quad \swarrow \quad \searrow \quad \swarrow \quad \searrow \\ z = bc + ac + ab \longrightarrow \text{1-term} \end{array}$$

One term can be used more than once (we cannot simplify one term at a time).


Implicant of a function

- Product term that can be part of a S-O-P expression of a function
- Product term that "covers" some minterms of a function

Minimization summary

- Karnaugh maps (manual)
 - Tedious and error-prone for 5 or 6-input functions. Unfeasible for >6 .
- Quine-McCluskey
 - Not feasible for a large number of inputs.
 - Computational time increases exponentially with n. of inputs (32 inputs $\rightarrow \sim 10^{15}$ prime implicants)
- Alternative: Heuristic logic minimizers
- Implemented in logic synthesis tools

Manual design process (summary)

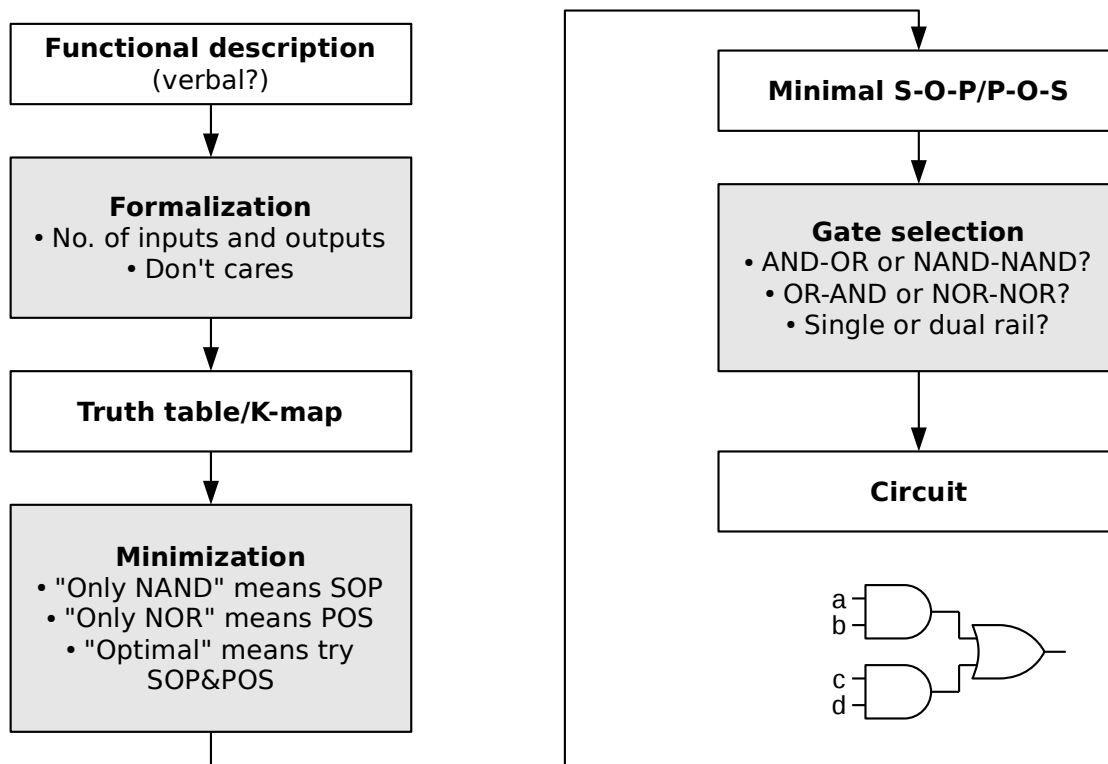

Design example

Design a combinational circuit with four inputs (x_3, x_2, x_1, x_0) that represent the bits of a BCD digit X , and two outputs (c_1, c_0) that represents the bits of a magnitude C , where C is the quotient of the division $X/3$.


E.g. if $X=7 \rightarrow C=2$, that is, $(x_3, x_2, x_1, x_0)=(0, 1, 1, 1) \rightarrow (c_1, c_0)=(1, 0)$

Design the circuit using a minimum two-level structure of only NAND gates.

Contents


- Logic functions
- Boolean algebra
- Expression minimization
- Don't cares
- **Functional analysis**
- **Timing analysis**

Functional analysis

 


- Method. Starting at primary inputs:
 - For each gate with known inputs, calculate the equation at the gate's output.
 - Repeat until the equations of all circuit outputs are known.
 - Convert to a more useful representation: truth table, K-map, ...
 - Give a verbal description of the operation (if possible).


Timing analysis

 
 
$$\begin{aligned}
 I1 &= \bar{x} \\
 I2 &= \bar{z} \\
 A1 &= I1 I2 \\
 A2 &= x y z \\
 f &= A1 + A2
 \end{aligned}$$


 
$$\begin{aligned}
 I1 &= \bar{x} \\
 I2 &= \bar{z} \\
 A1 &= I1 I2 \\
 A2 &= x z \\
 f &= A1 + A2
 \end{aligned}$$



Method:

- For every gate: equations of the output as a function of the inputs.
- Substitute constant input values (DO NOT SUBSTITUTE ANYTHING ELSE)
- Draw node curves from primary inputs to the outputs. Delay every output transition by the gate's delay time (simple model: same delay for every gate: Δ)