

---

# Unit 1.5. Electronic circuits and logic families

Digital Electronic Circuits  
E.T.S.I. Informática  
Universidad de Sevilla

Jorge Juan-Chico <jjchico@dte.us.es> 2010-2020

You are free to copy, distribute and communicate this work publicly and make derivative work provided you cite the source and respect the conditions of the Attribution-Share alike license from Creative Commons.

You can read the complete license at:


<http://creativecommons.org/licenses/by-sa/4.0>

# Contenidos

---

- Electronic circuits
  - Charge and conductors
  - Electronic devices
  - Electric circuits
  - Semiconductors
  - Technology: discrete and integrated devices
- Logic families
  - Digital circuits
  - Gates and logic operators
  - Logic families
  - Electrical and switching parameters

# Conductors and charge carriers

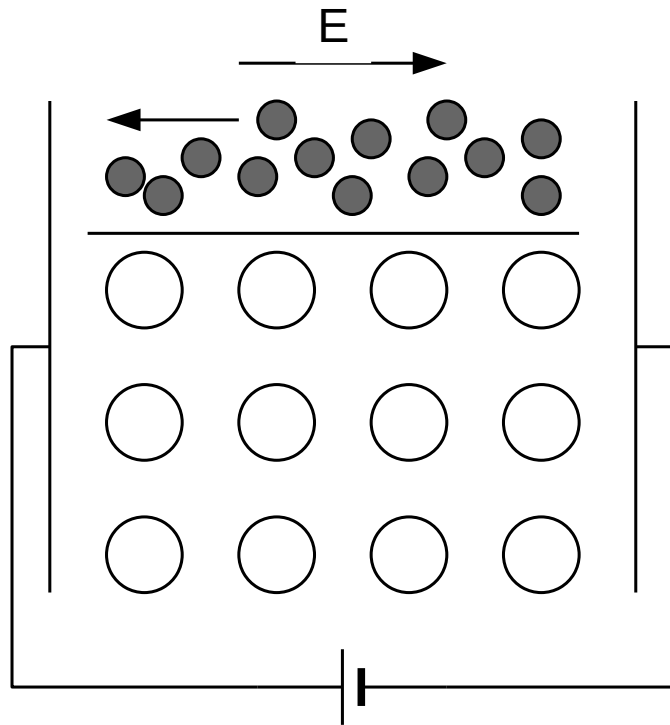


- Metal atoms
- Free electrons

- Conductors charge carriers can be positive (+) or negative (-)
- Most typical charge carriers are “free” electrons (-) in metals.
- When an electric field (E) is applied, electrons move accordingly.
- Electric fields exist whenever an electric potential difference (voltage) is applied.
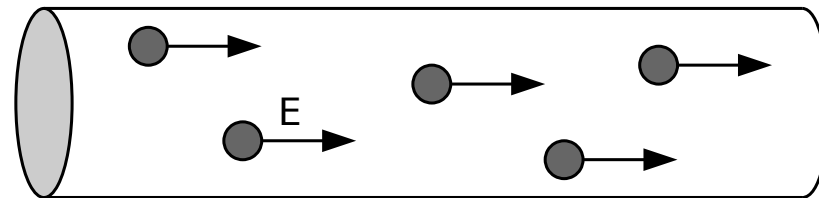
# Basic conductor properties


- Conductors in electrical circuits
  - Typically wire-shaped
  - Charge (and electric field) is confined inside the conductors
- Charge does not accumulate inside conductors: conductors remain neutral.



# Electrical magnitudes


- Voltage: potential difference between two points in the circuit (Volts [V]).
  - Electric field (electric force) points from high to low voltage areas.
  - Positive charges move to lower voltage, negative charges to higher voltage (lower energy in both cases).
  - Current: charge per unit time crossing the conductor's section
  - Absolute voltage values do not exist. An arbitrary point is selected as zero voltage (ground node or GND).
- Current: charge per unit time crossing the conductor's section (Amperes [A]).
  - Same current in all sections of a conductor. Why?

$$I = \frac{dQ}{dt}$$

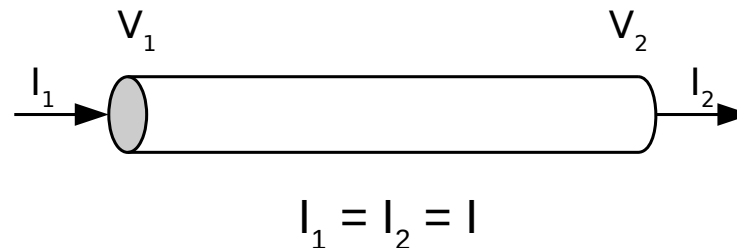
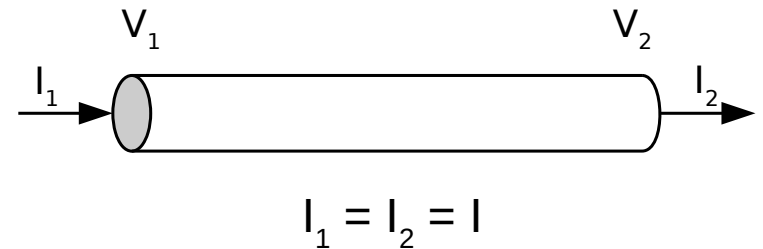
# Ohm's Law


- Ohms law
  - Resistance: relation between the voltage and current across the conductor.
  - Unit: Ohms  $[\Omega]=[V]/[A]$
- Ideal conductors ( $R=0$ )
  - Wires: metals used for connection in electronic circuits can be considered ideal conductors most of the time.
  - Consequence: same voltage across wires.



$$R = \frac{V_1 - V_2}{I}$$

$$R = 0 \Rightarrow V_1 = V_2$$

# Electronic devices

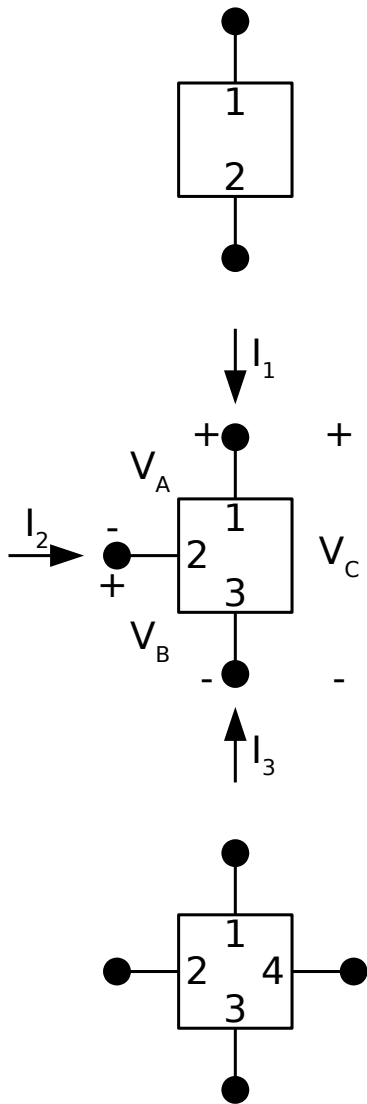


- Electronic elements with two or more terminals (connection points)
- Impose a relationship between the current and voltage across the terminals
- Net charge is not accumulated inside the devices:

$$- I_1 + I_2 + I_3 + \dots = 0$$

# Basic electronic devices


---

Resistor  
Ohm [ $\Omega$ ]

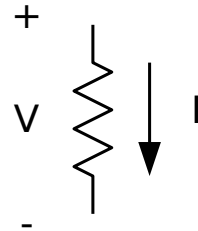


$$V = IR$$

Capacitor  
Farad [F]

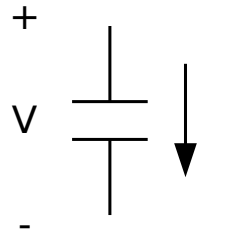

$$I = C \frac{dV}{dt}$$

Inductor  
Henry [H]

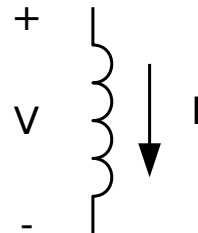


$$V = -L \frac{dI}{dt}$$



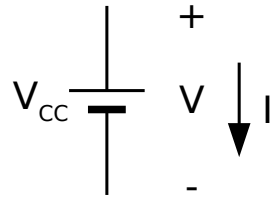
# Dispositivos básicos: fuentes ideales


Constant voltage source  
(power supply)  
(battery)




$$V = V_{CC}$$

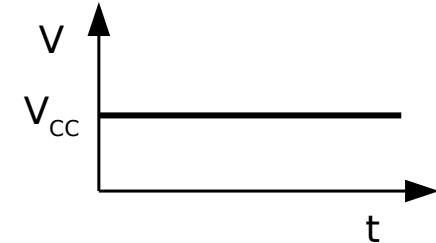


Variable voltage source

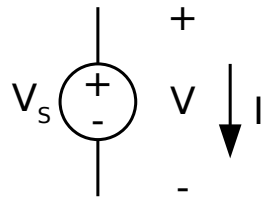


$$V = V_s(t)$$

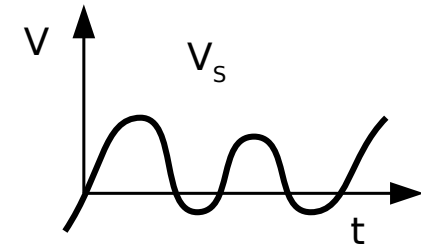

Variable current source

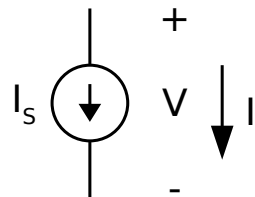


$$I = I_s(t)$$

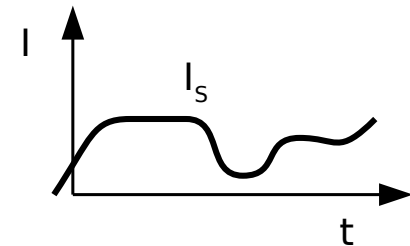

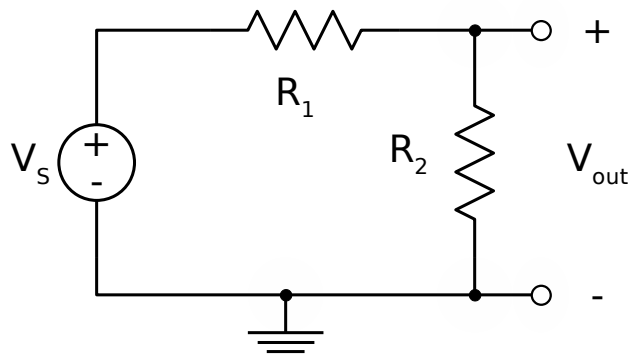
# Electric circuits

- Connection of devices with wires to achieve some properties or functionality.
- Node: connection between two or more devices.
  - Same voltage alongside a single node (ideal wire)



Voltage divider

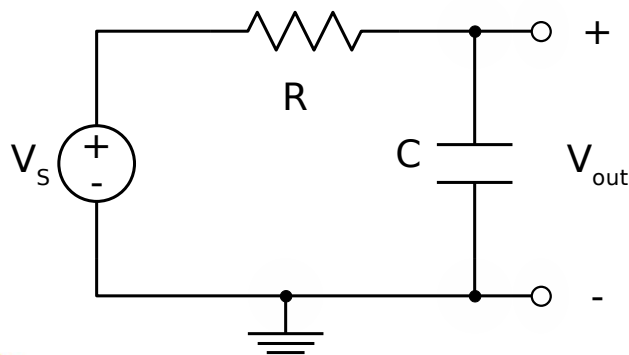

Low-pass filter

# Circuit analysis

---


- Circuit analysis is based on:
  - Device equations
  - Topological Equations (Kirchhoff laws)
- Kirchhoff laws
  - Current: the sum of the currents entering a circuit node is zero (charge does not accumulate in circuit nodes)
  - The sum of voltage drops along any close path is zero.

# Types of circuit analysis

---




- Static analysis (DC):
  - All magnitudes and sources are constant.
  - The solution is derived from algebraic equations.
- Transient analysis
  - Considers variable sources and the evolution of circuit's magnitudes with time.
  - In general, the solution implies resolving differential equations :(
- Frequency analysis (AC)
  - Solves the circuit for sinusoidal signals.
  - Simplified resolution thanks to the use of specific mathematical tools (Laplace's Transform).
  - Obtains the circuit response as a function of the signal's frequency.

# Circuit analysis. Example

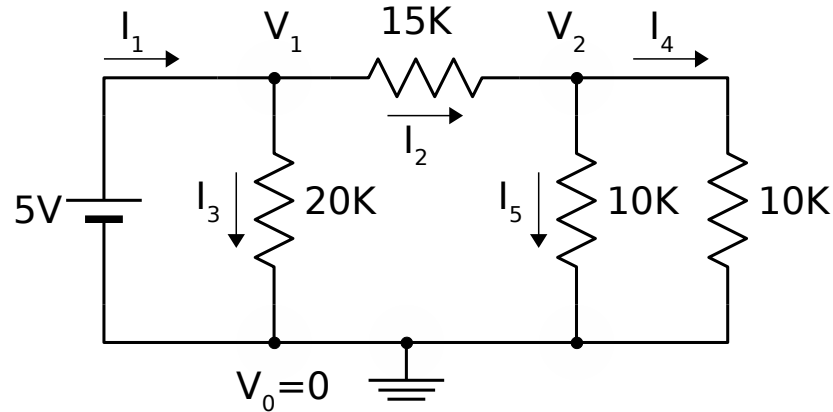

Static analysis (DC)

Simulation

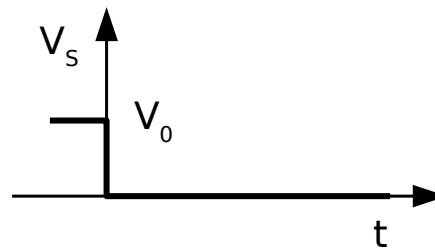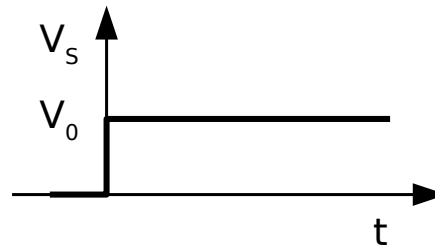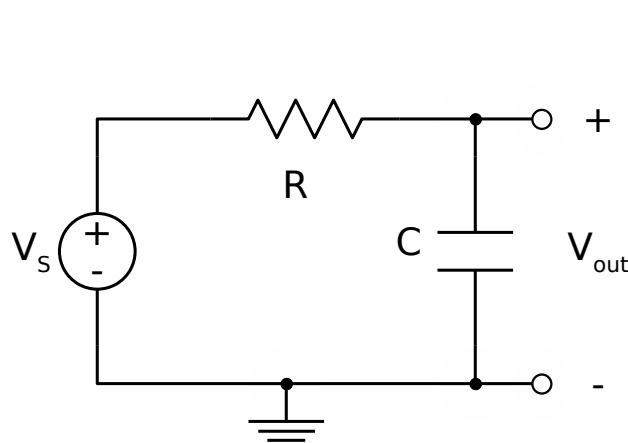


Transient analysis

Simulation

# Power


---

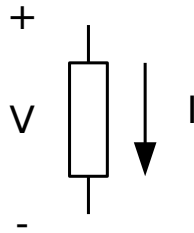

$$P = VI$$

- Consumed energy per unit time
- Power is a key point in current electronics.
  - Portable devices (batter duration)
  - Dissipation (put a big fan!)
  - Environment (climate change)
- Power is consumed (dissipated) every time some current goes from a higher to a lower potential.
- Power can be negative
  - In this case, the device is "producing" power to be consumed in the circuit (e.g. power supply)


# Semiconductor devices (intrinsic)

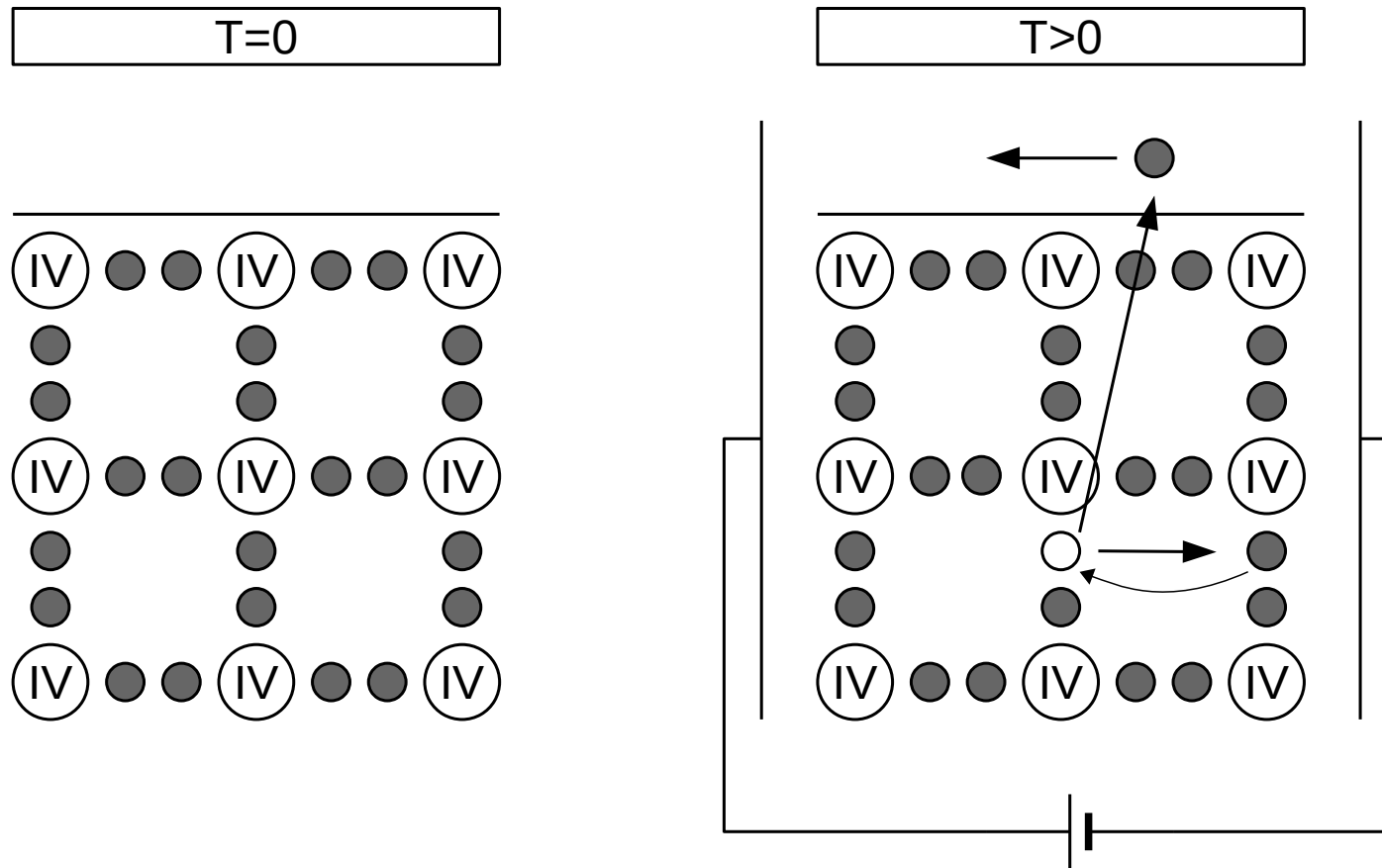

- ⓐ Group IV atom (Si)
- Electron (-)
- Hole (+) (left by the electron)


# Semiconductor devices (doped) (T=0)

n-type

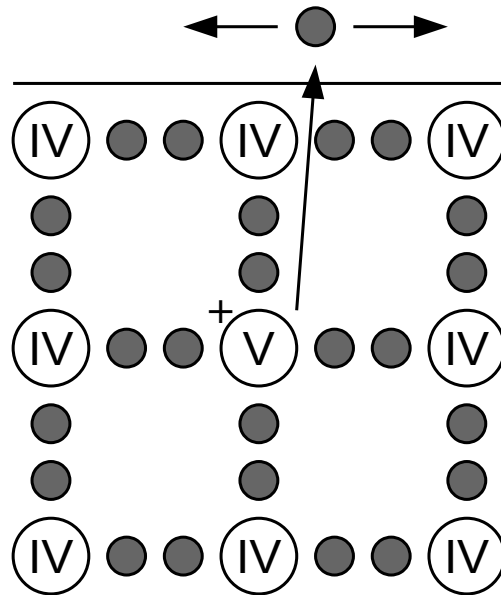

good conductor

p-type

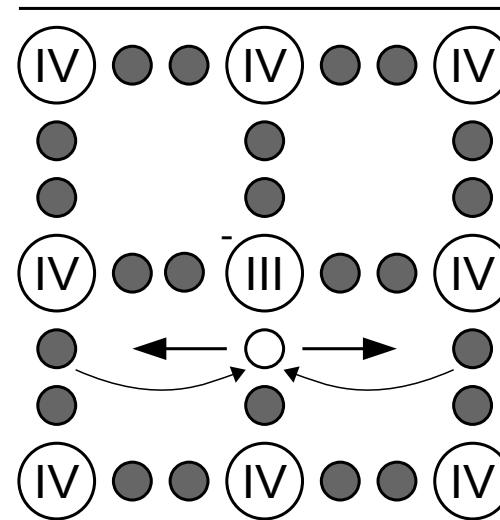

good conductor

- Electron (-)
- Hole (+) (left by the electron)

- ⓐ Group IV athom (Si)
- ⓑ Group V athom (P, As)
- ⓒ Group III athom (B, Ga)









# Semiconductors nice properties



---

- Conductance depends on temperature, light, etc.
  - Temperature sensors
  - Light sensors
  - Solar cells
  - ...
- Conductance can be controlled by doping.
- Type of carrier (+ or -) can be controlled by doping (P or N).
- Nice devices can be created by combining different types of semiconductors (P+N).
  - Electrical: selective conductivity.
  - Optical: light emission.
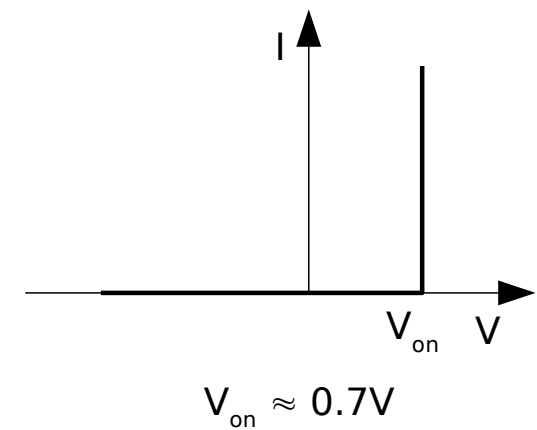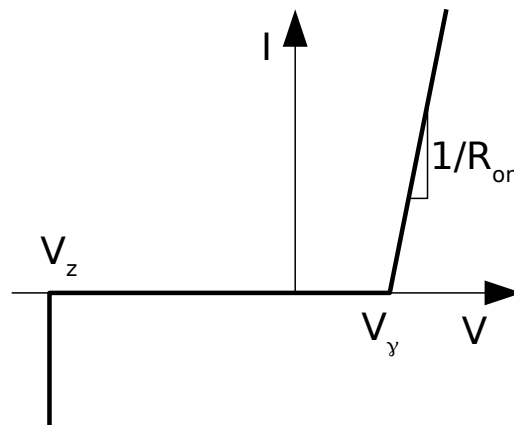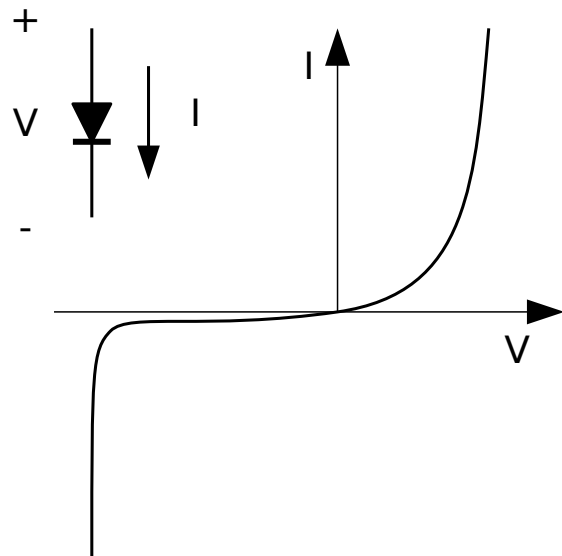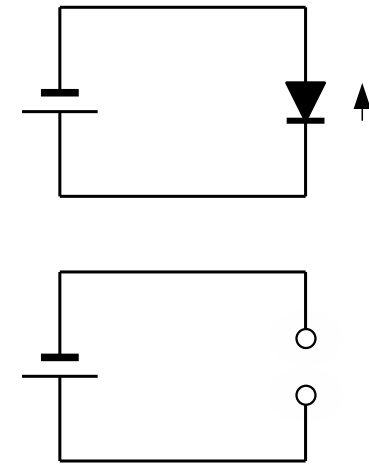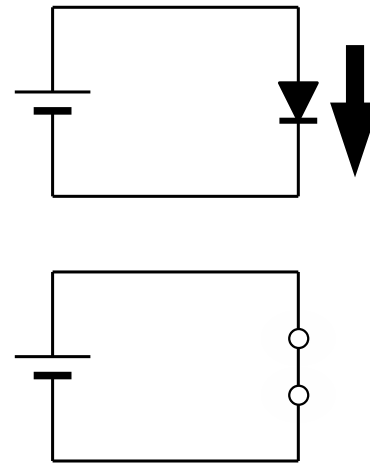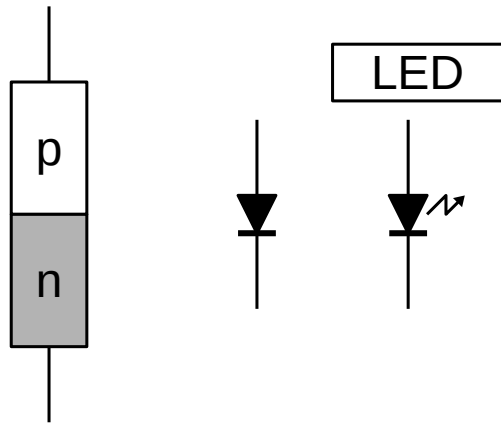
# Diodes and Light-Emitting Diodes (LED's)



# Bipolar transistor

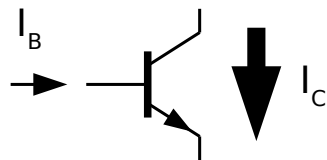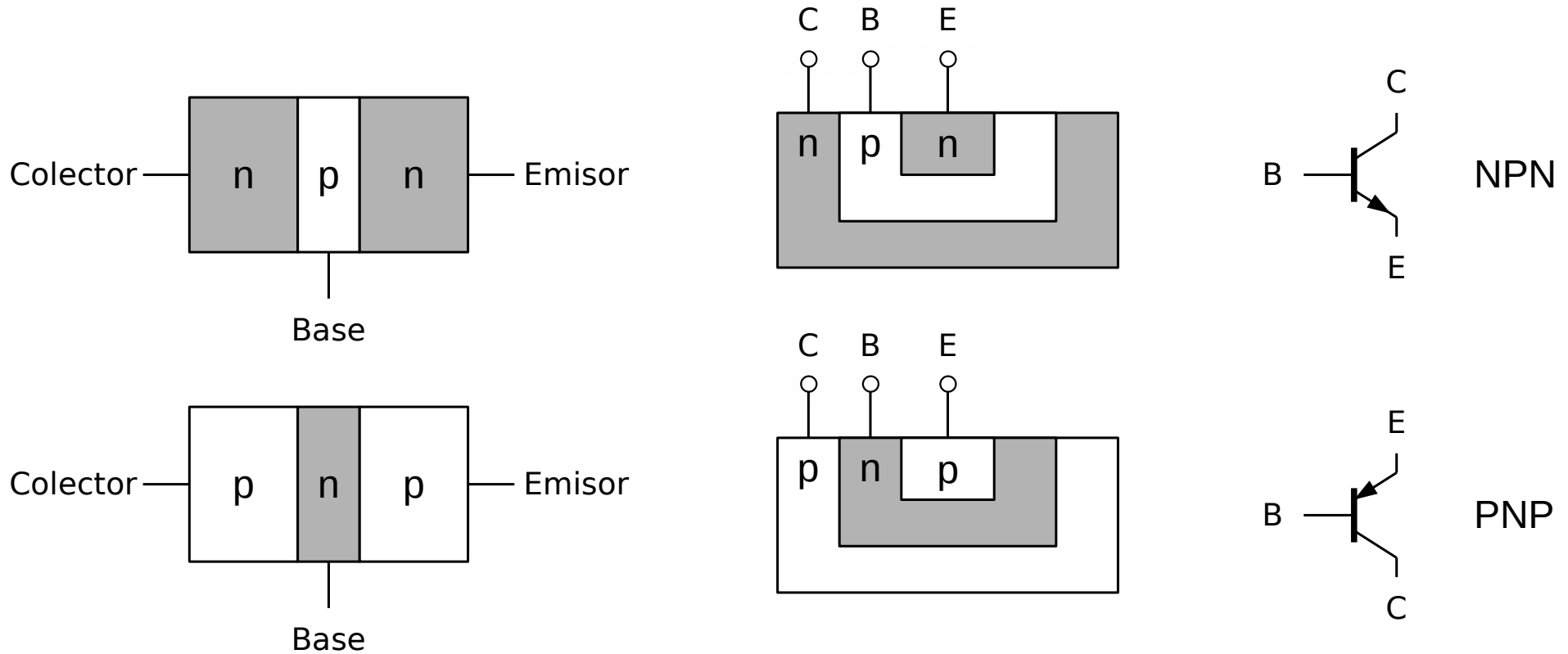


$$I_C = \beta I_B$$

$$\beta \approx 100$$






A small current through B-E allows a big current to flow through C-E.

Direct use: amplifier.
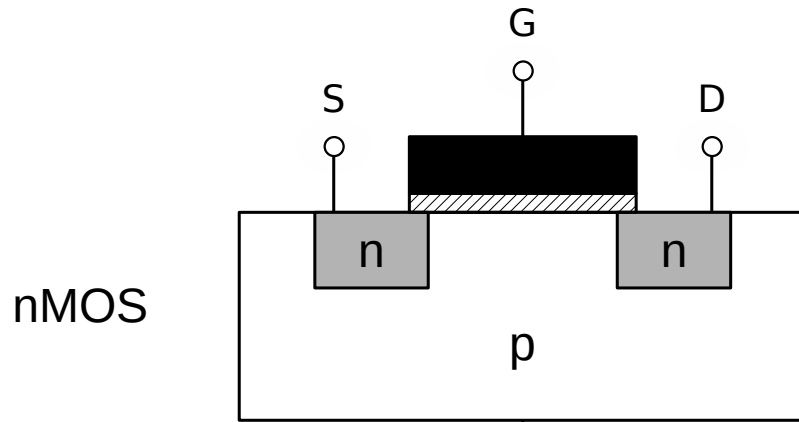
# Field Effect Transistors (E.g.: MOSFET's)



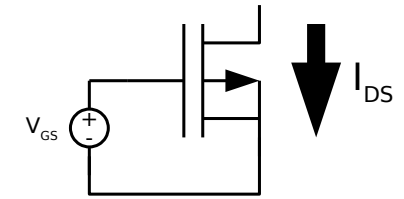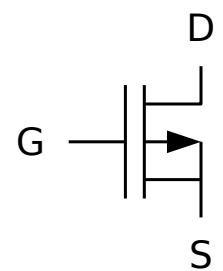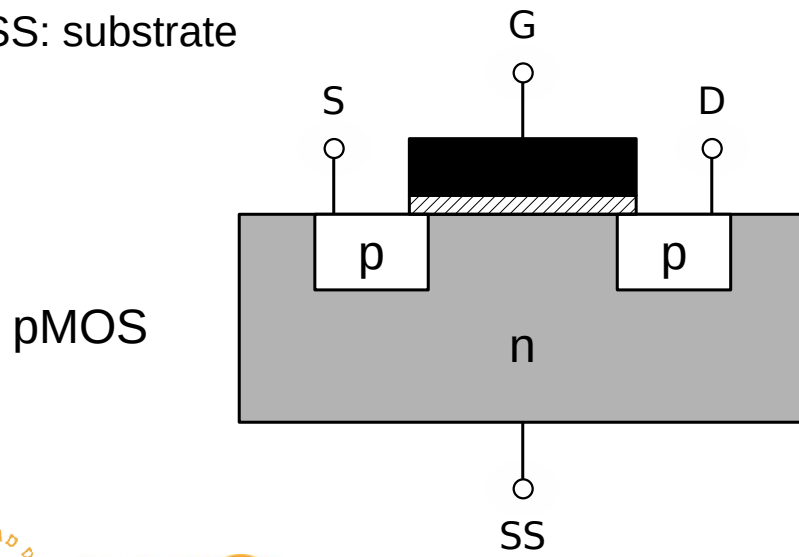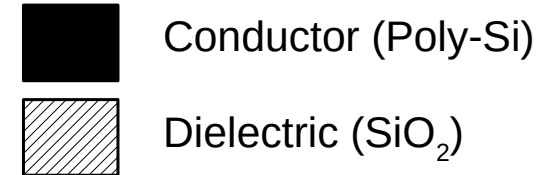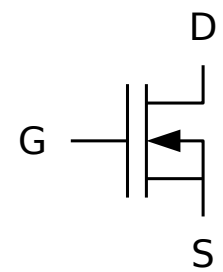G: gate  
S: source  
D: drain  
SS: substrate




A small voltage between G and S allows a big current to flow from D to S.

Applications: amplifier, sensors, power control, etc.

# Transistors demo


$$V = IR \quad I = \frac{V}{R}$$

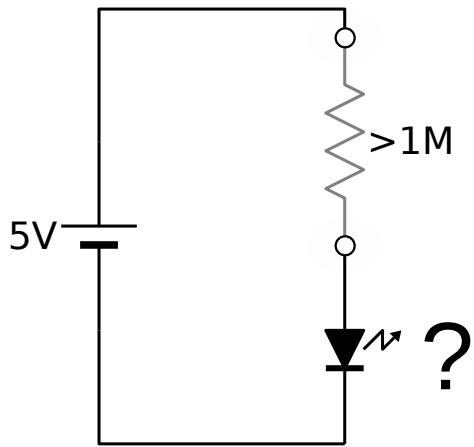


$$I_D = I_R \approx 0$$

$$I_C = \beta I_B$$

$$\beta \approx 100$$

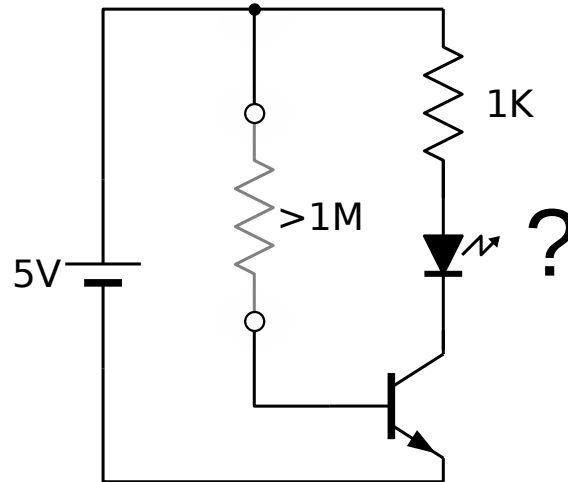

$$I_D = I_C \approx 100 I_R$$

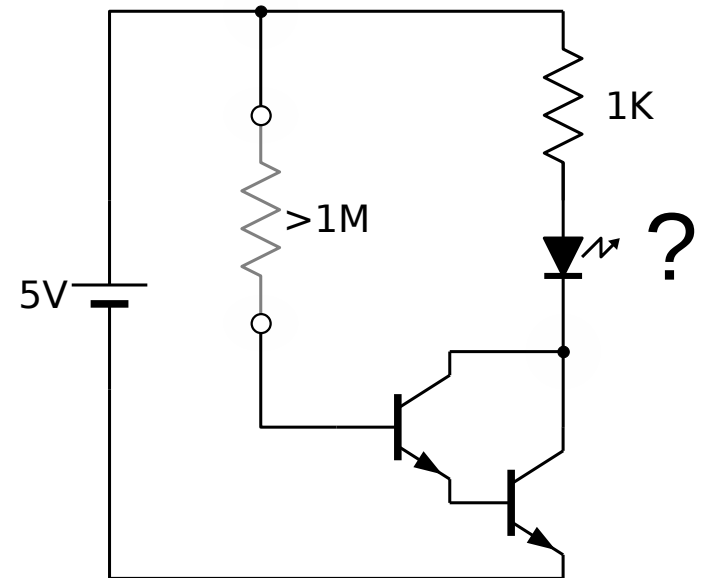




$$I_D \approx 10000 I_R$$

# Electronic technology


---

- Discrete components
  - Devices are fabricated one by one
  - Normally, they are soldered in printed circuit boards (PCB's)
- Integrated circuits (chips, IC's)
  - Several devices (mostly transistors) are fabricated at the same time over a common substrate.
  - Really big numbers: 10-500 million! devices in the same chip.
  - Most of today's electronics is done as IC's
- Types of IC's
  - Application specific (ASIC)
  - Programmable (E.g. FPGA)

# Electronic devices

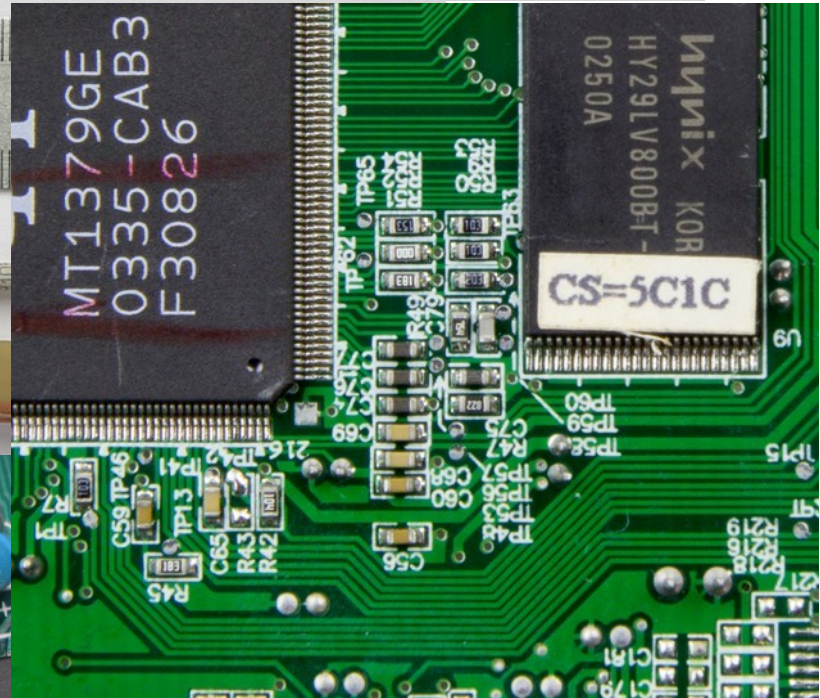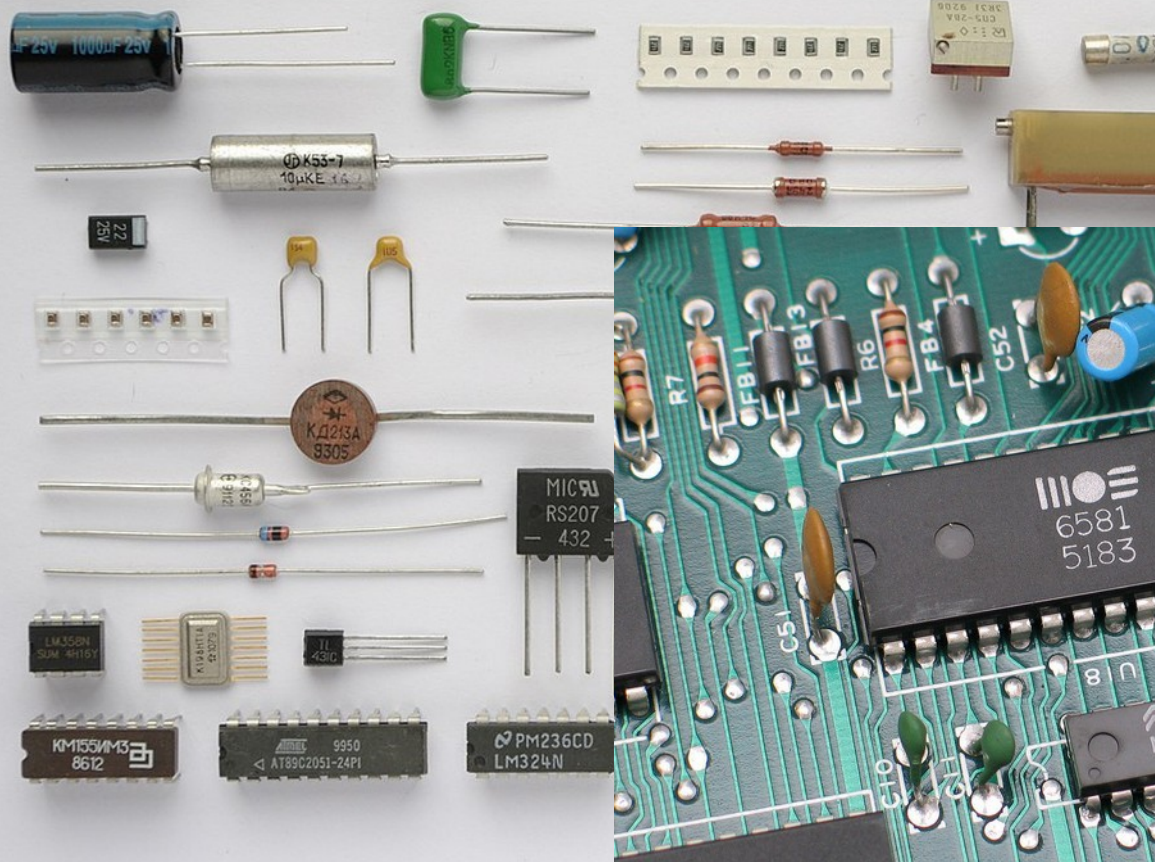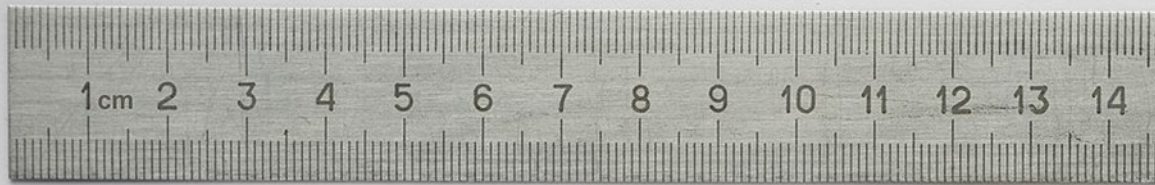



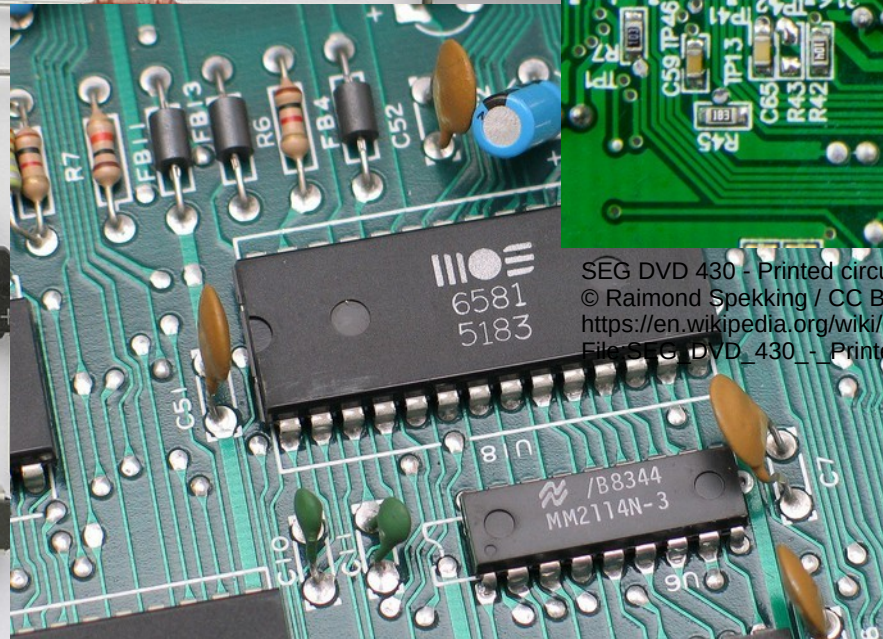
SE&G DVD 430 - Printed circuit board (2003)  
 © Raimond Spekking / CC BY-SA 4.0 (via Wikimedia Commons)  
[https://en.wikipedia.org/wiki/Printed\\_circuit\\_board#/media/File:SE&G\\_DVD\\_430\\_-\\_Printed\\_circuit\\_board-4276.jpg](https://en.wikipedia.org/wiki/Printed_circuit_board#/media/File:SE&G_DVD_430_-_Printed_circuit_board-4276.jpg)



Commodore 64 PCB (1980)  
 By Christian Taube - Own work, CC BY-SA 2.5,  
<https://commons.wikimedia.org/w/index.php?curid=1503038>

By Kae - Own work, Public Domain  
<https://commons.wikimedia.org/w/index.php?curid=655329>

# Integrated circuits

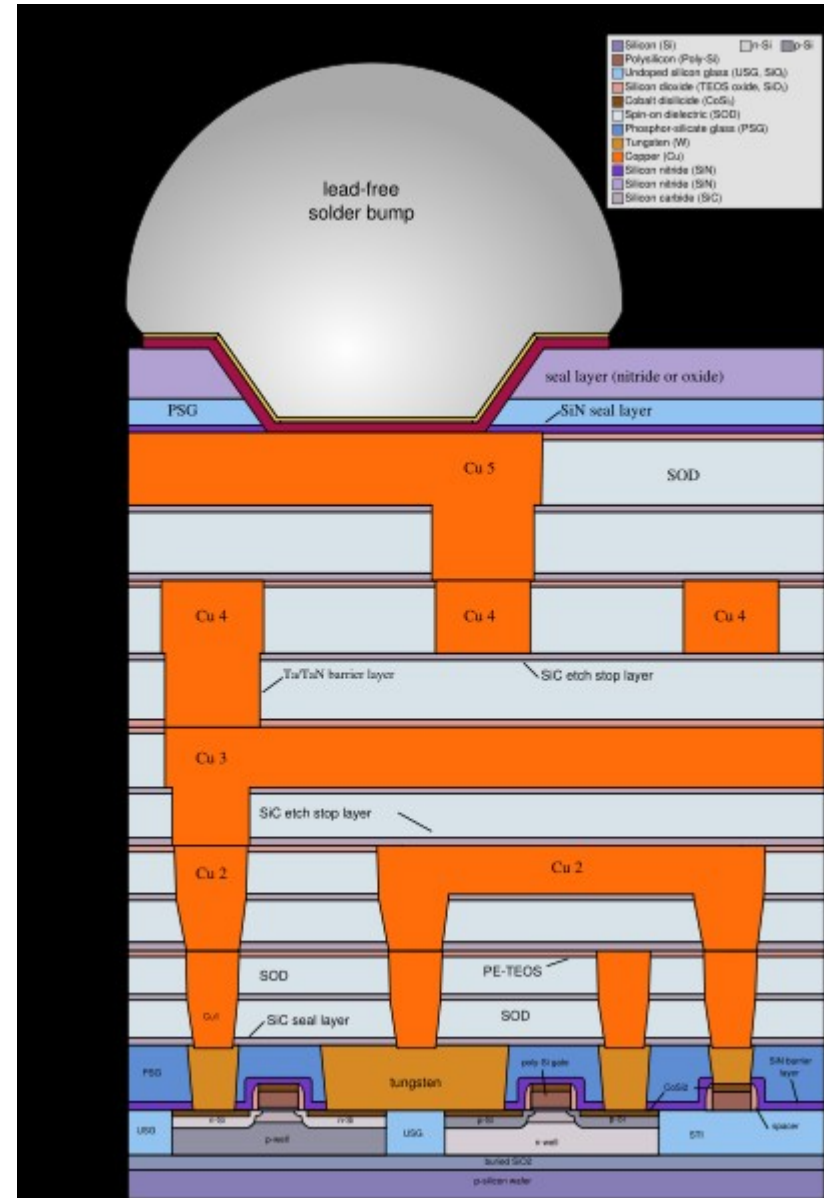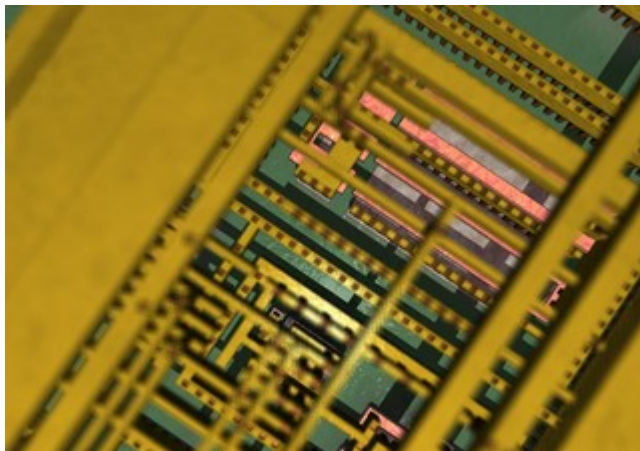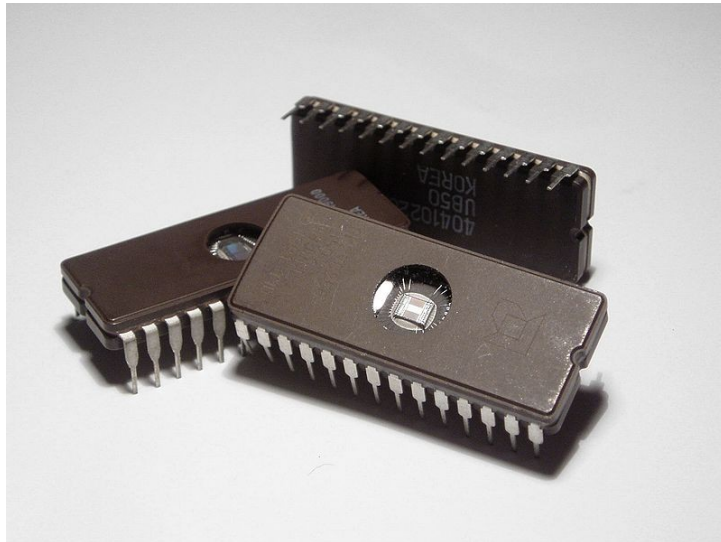


[http://en.wikipedia.org/wiki/Integrated\\_circuit](http://en.wikipedia.org/wiki/Integrated_circuit)



# Integrated circuits. Types

Application Specific IC (ASIC)



Intel Pentium

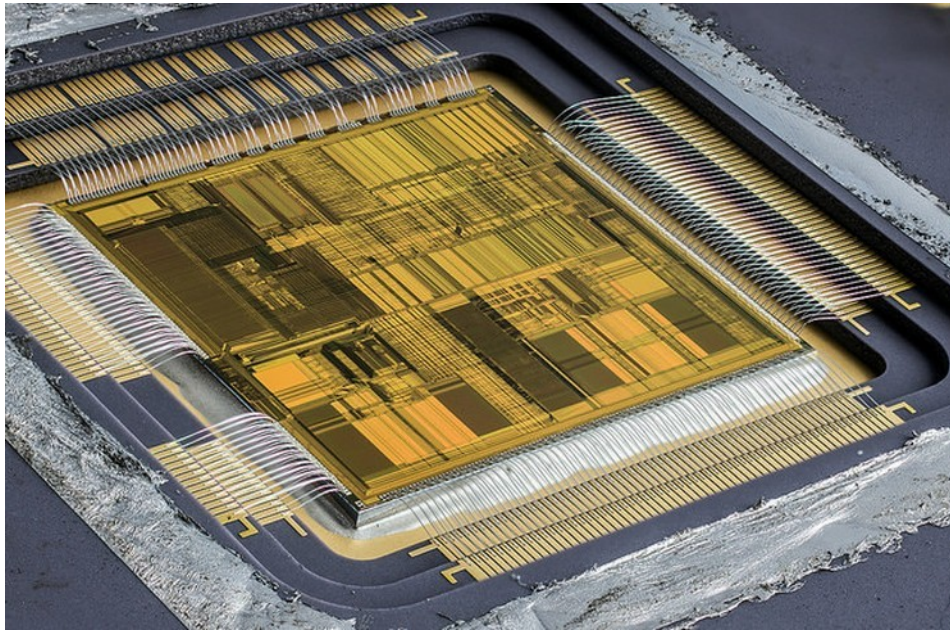

Dominio Público  
<https://www.flickr.com/photos/130561288@N04/16637740870>

Programmable (ej. FPGA)

Xilinx XC4010-6

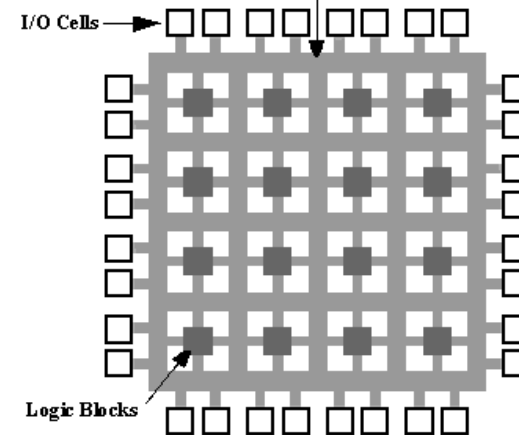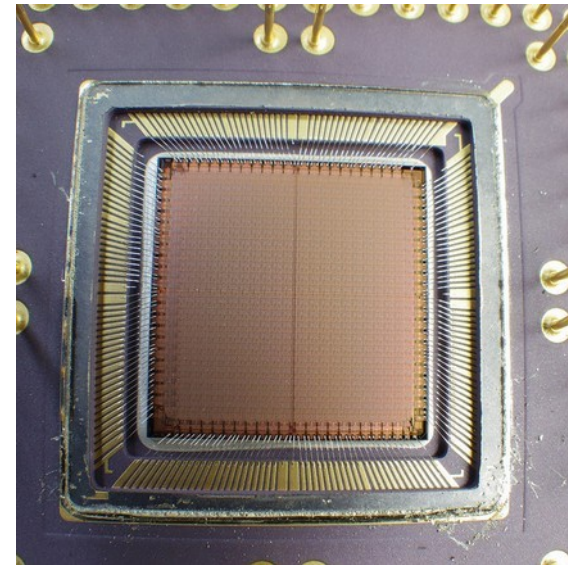

<http://commons.wikimedia.org/wiki/File:Fpga1a.gif>

Xilinx XC4010-6. Dominio Público  
<https://www.flickr.com/photos/34923408@N07/22054207552/>

# Integrated Circuits. Generations

Name	Meaning	Year	No. tt	Comment
SSI	Small-scale integration	1964	1 a 10	Military and space applications
MSI	Medium-scale integration	1968	10 a 500	Consumer electronics
LSI	Large-scale integration	1971	500 a 20000	Microprocessors and integrated memories
VLSI	Very large-scale integration	1980	20000 a 1M	Advances microprocessors and memories. Need Design Automation (DA)
ULSI	Ultra-large-scale integration	1984	> 1M	System on Chip (SoC)


# Evolution

Vacuum tube



By Kguirmela - Own work, CC BY 3.0  
<https://commons.wikimedia.org/w/index.php?curid=3820451>

Transistors

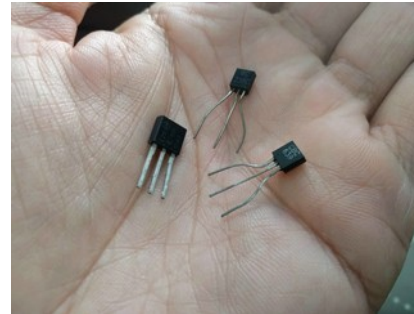

Integrated Circuit  
Intel Pentium IV (~50Mtt)



ENIAC (1946)



By Unidentified U.S. Army photographer, Public Domain  
<https://commons.wikimedia.org/w/index.php?curid=978770>

IBM 360 Model 20 (1966)



By Ben Franske - DM IBM S360.jpg on en.wiki, CC BY 2.5  
<https://commons.wikimedia.org/w/index.php?curid=1189162>


Laptop (2018)



By Vostrouser - Own work, CC0  
<https://commons.wikimedia.org/w/index.php?curid=47766991>
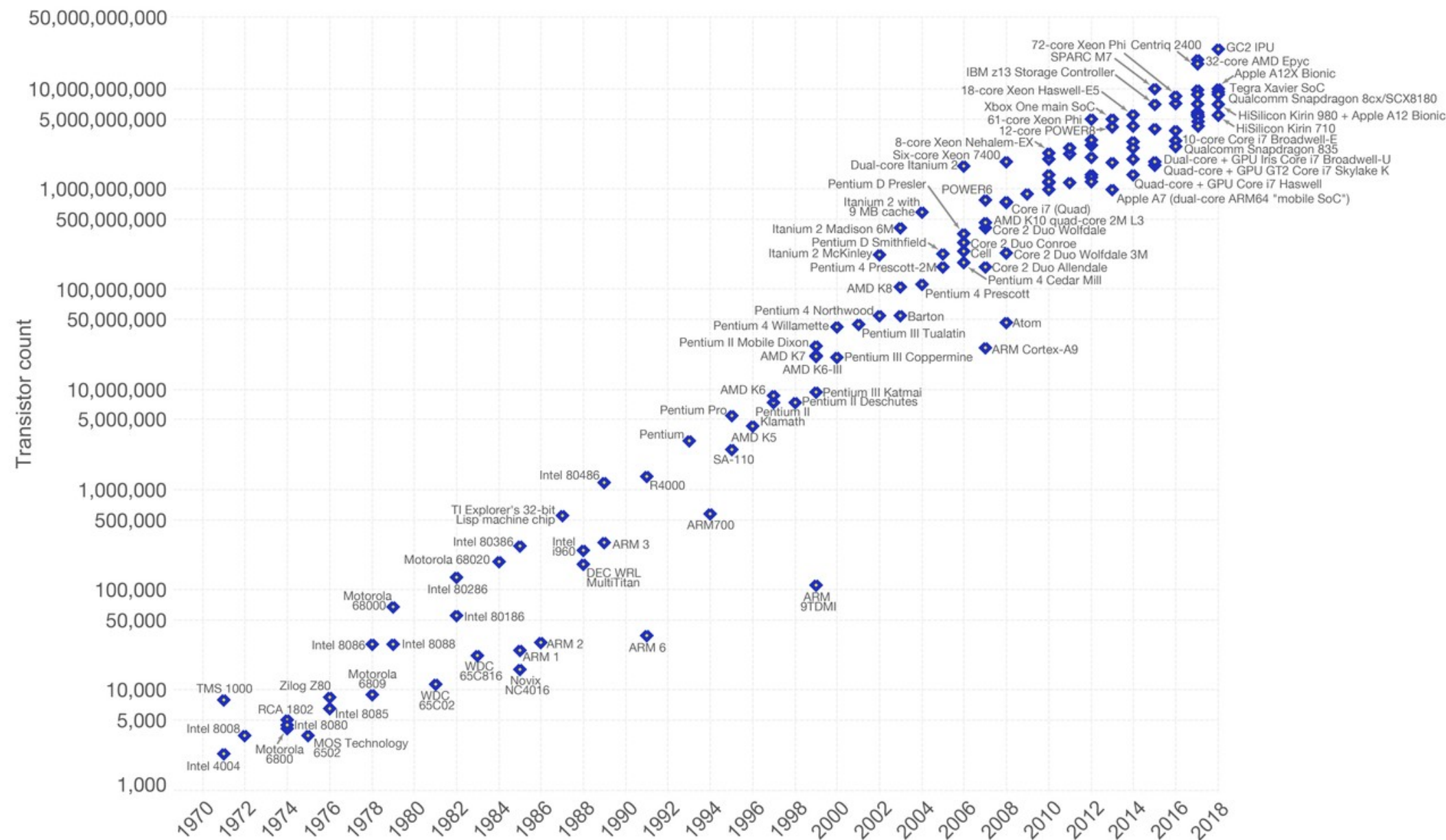
# Moore's Law – The number of transistors on integrated circuit chips (1971-2018)

Moore's law describes the empirical regularity that the number of transistors on integrated circuits doubles approximately every two years. This advancement is important as other aspects of technological progress – such as processing speed or the price of electronic products – are linked to Moore's law.



Data source: Wikipedia ([https://en.wikipedia.org/wiki/Transistor\\_count](https://en.wikipedia.org/wiki/Transistor_count))

The data visualization is available at [OurWorldinData.org](https://www.ourworldindata.org). There you find more visualizations and research on this topic.


Licensed under CC-BY-SA by the author Max Roser.

# Digital circuits and logic families


---

- Digital circuits
- Logic gates and logic operators
- Logic families
- Electrical parameters
- Switching parameters

# Digital circuits

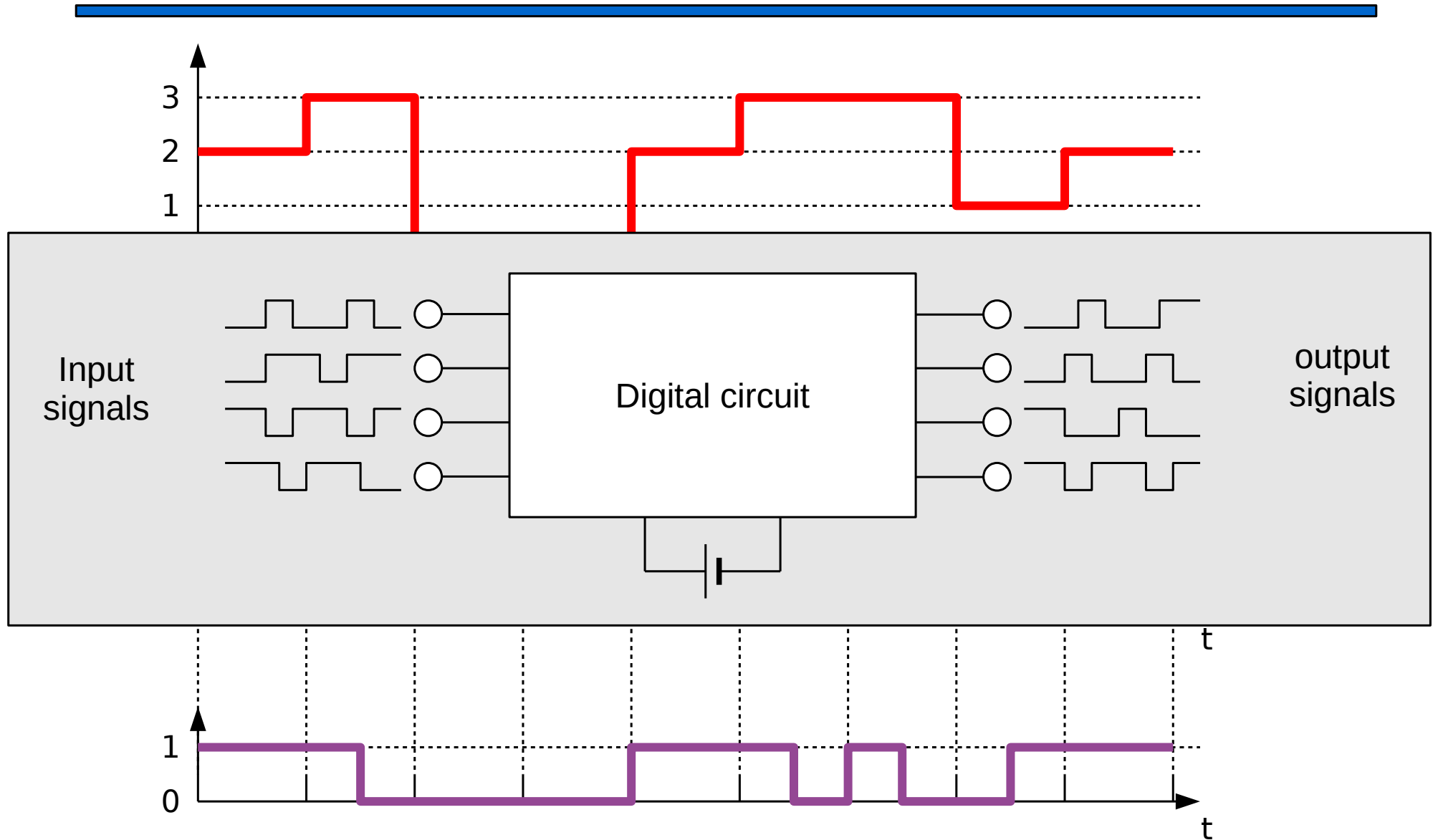


# Digital circuits. Logic levels

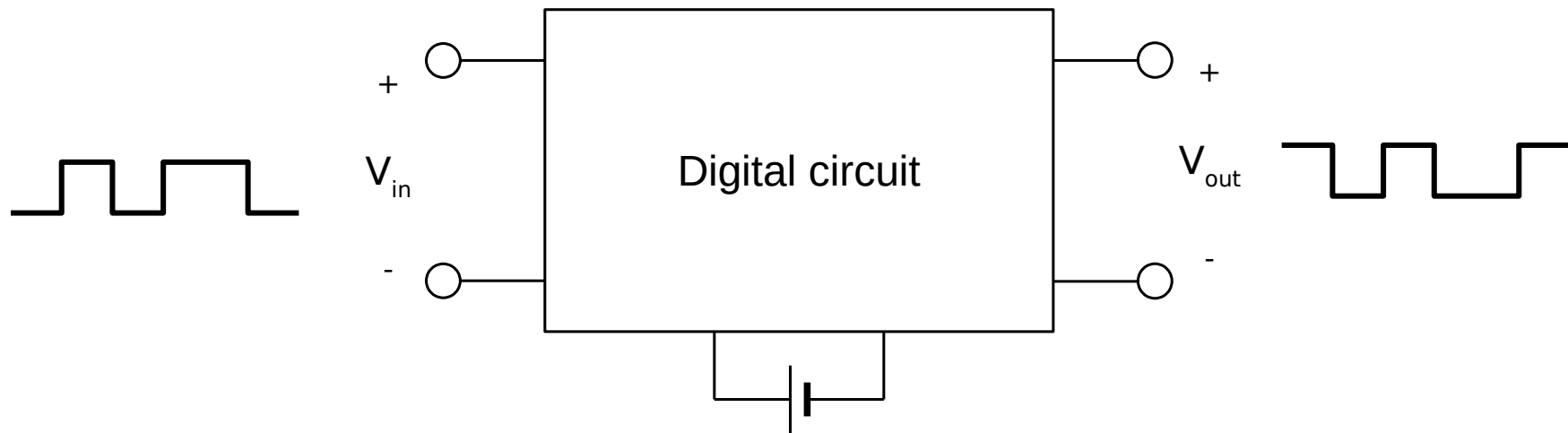





Electric value ( $V_x$ ) vs. logic value (X)

Ejemplo: 3,3V

$V_x$	X
$\sim 0V$	0
$\sim 3,3V$	1

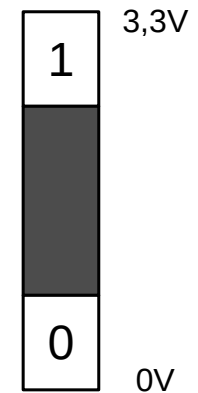

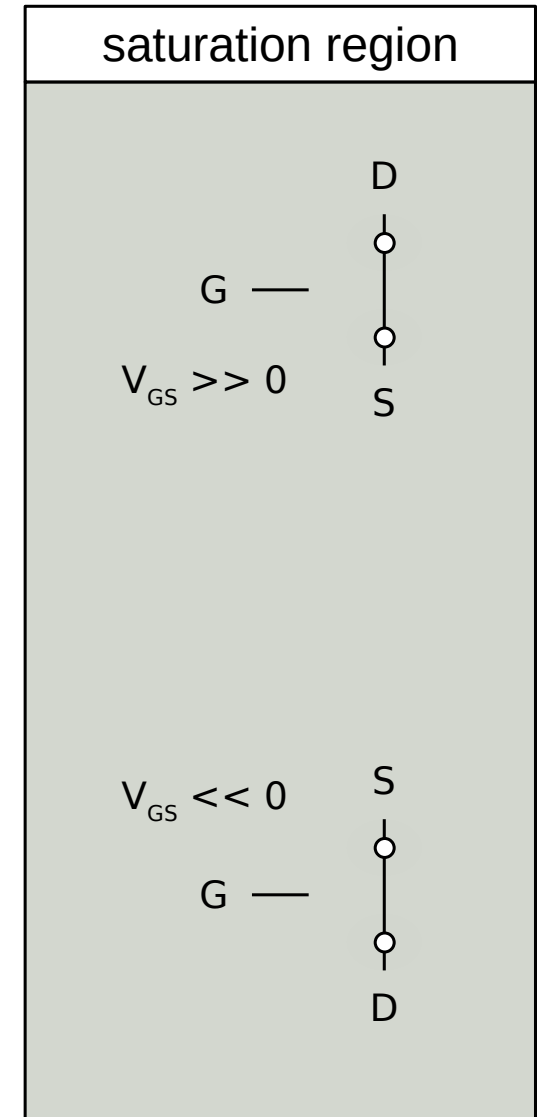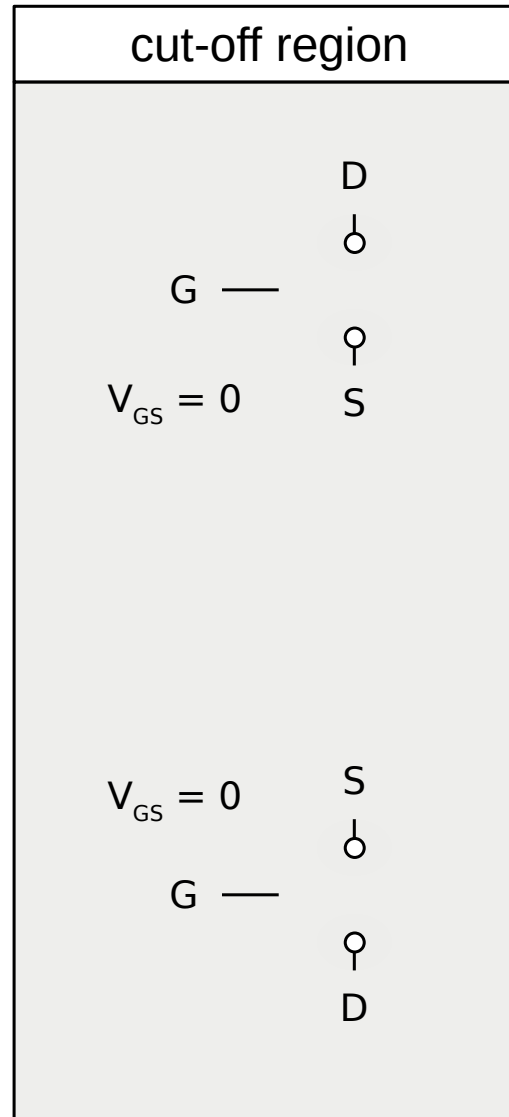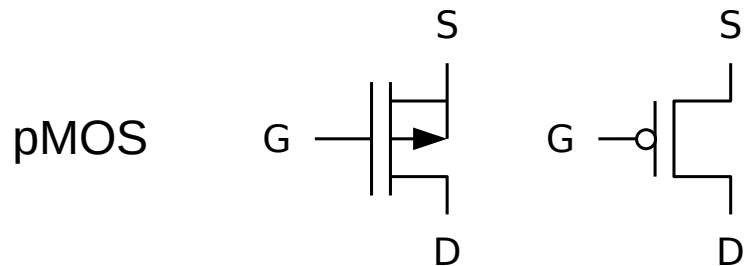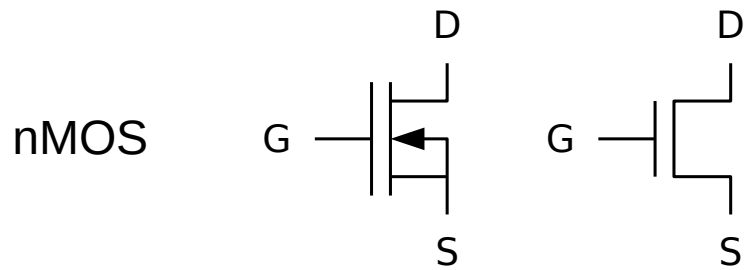
# Transistors in switching mode (MOS example)






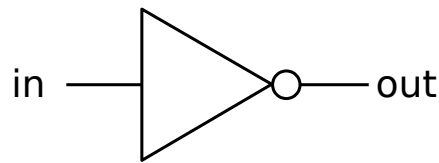
# Logic gates. CMOS Inverter

- Logic gates perform simple operations on digital data.
- The simplest (non identical) operation is “inversion”, implemented by the inverter gate.




in	out
0	1
1	0

Simulación

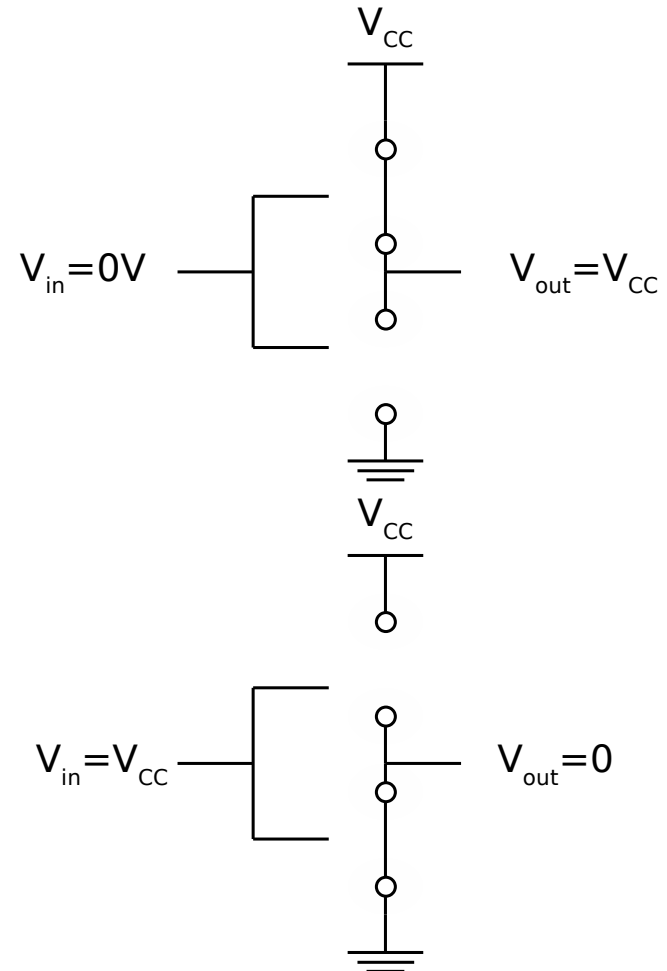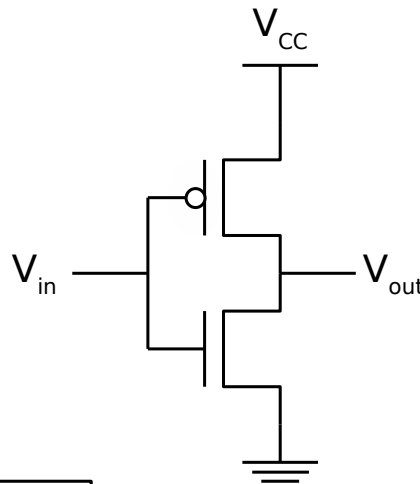


# Logic gates and logic operators

AND

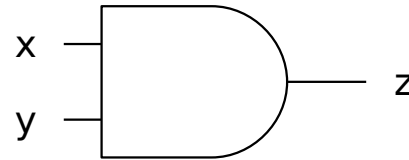


x y	z
0 0	0
0 1	0
1 0	0
1 1	1

NAND

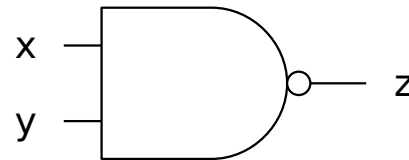


x y	z
0 0	1
0 1	1
1 0	1
1 1	0

OR

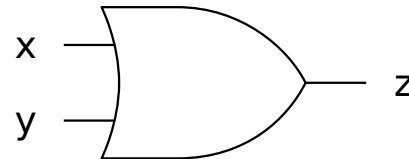

x y	z
0 0	0
0 1	1
1 0	1
1 1	1


NOR

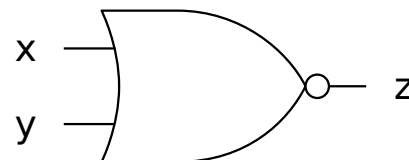

x y	z
0 0	1
0 1	0
1 0	0
1 1	0


# Logic gates and logic operators

XOR

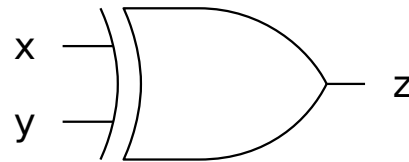

x y	z
0 0	0
0 1	1
1 0	1
1 1	0



XNOR

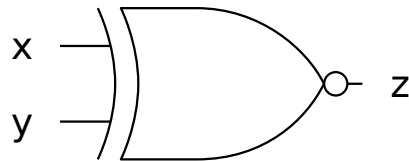

x y	z
0 0	1
0 1	0
1 0	0
1 1	1



CMOS gates are “naturally inverting”  
(INV, NAND, NOR, ...)

# Logic gates. CMOS NAND

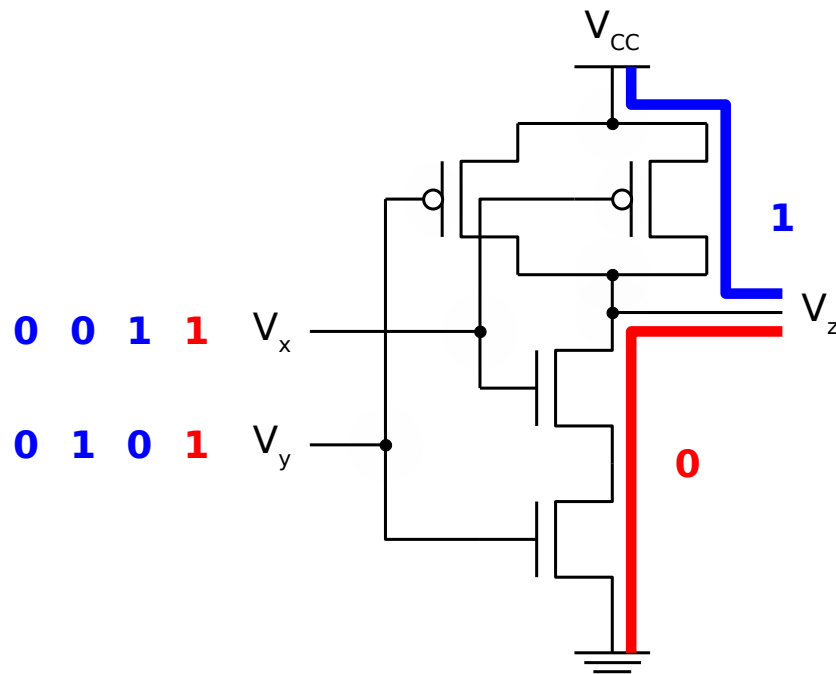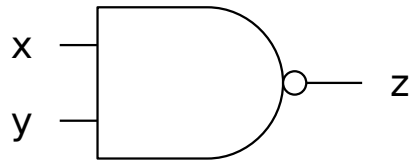

Simulation

# Logic Gates. CMOS NOR

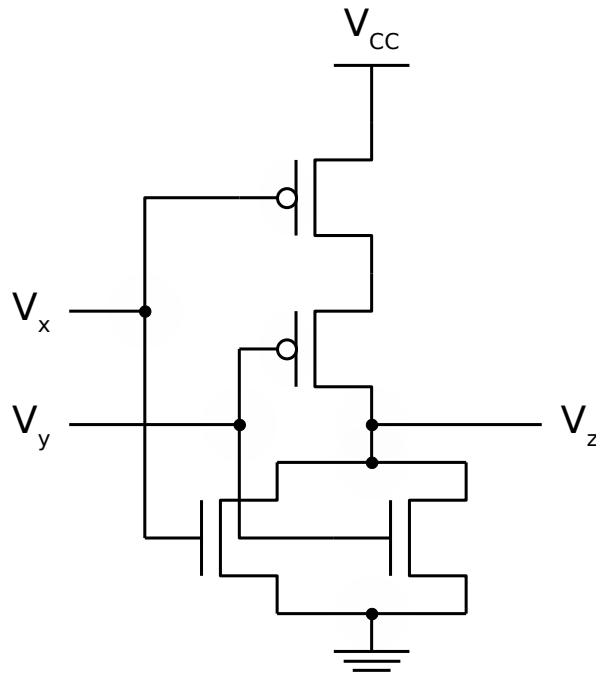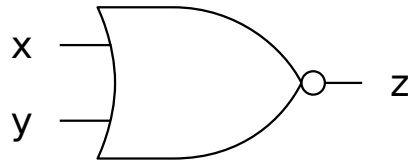

Simulation

# Examples: digital interface

---

- Simple digital signal generation
  - Switch
  - Push button
  - Variable resistance sensor:
    - light, temperature, humidity, etc.
  - Sensor sensitivity adjustment
- Simple digital signal perception
  - LED + resistor
  - Buzzer
  - Etc.

# Example


- Simple alarm system with a NAND gate

- On/off switch
- Contact sensor
- Alarm indicator (LED, etc.)

- Modifications

- Alarm when sensor is off
- Activate something bigger
  - Relay
  - Light
  - Engine
  - ...

x	y	NAND
0	0	1
0	1	1
1	0	1
1	1	0

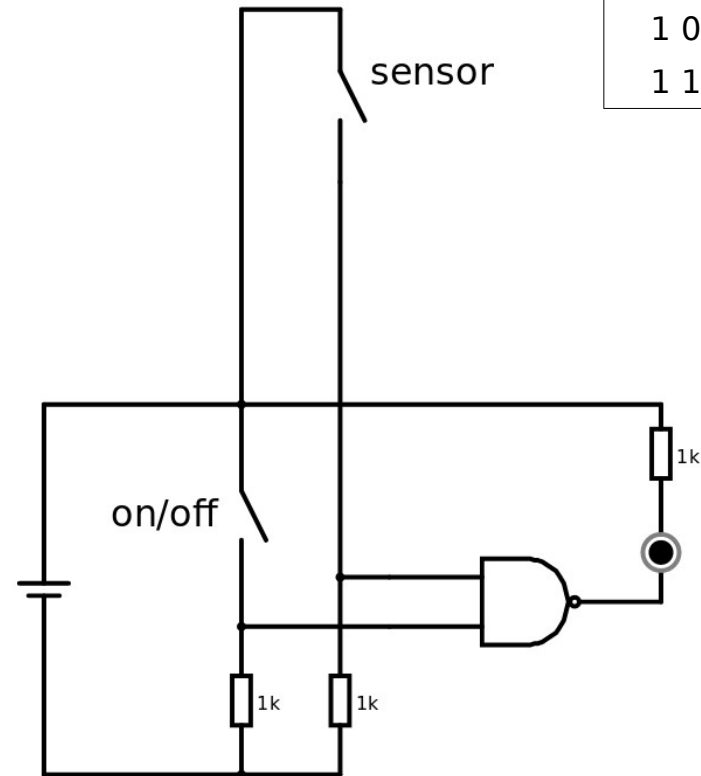

Simulation

# Logic families

---

- Logic gates are fabricated using different technologies (Bipolar, CMOS, ...) and different techniques.
- Logic family: set of gates sharing the same technology and similar design techniques
  - Gates in a family are compatible: will operate correctly when connected to each other.
  - Share similar electrical and dynamic parameters.
- Some logic families are compatible with others.
- Specially relevant when working with SSI and MSI devices (7400 series)







# Logic families

---

- Bipolar
  - ECL (Emitter-coupled-logic, 1962): first logic family available in integrated circuits.
  - DTL (Diode-Transistor-Logic, 1962).
  - RTL (Resistor-Transistor-Logic, 1963): used in the Apollo guidance computer (first CPU built from IC's).
  - TTL (Transistor-transistor logic): very popular. Many improvements since 1963. E.g. 74 series.
    - LS TTL: very popular low-power variant
- CMOS
  - E.g. HC logic. Compatible with TTL. E.g. 74HC series
  - Most extended technology nowadays in IC's
  - Better noise margins, lower static consumption, cheaper, but slower.
- BiCMOS
  - Combines CMOS inputs with TTL drivers
  - Includes various logic families
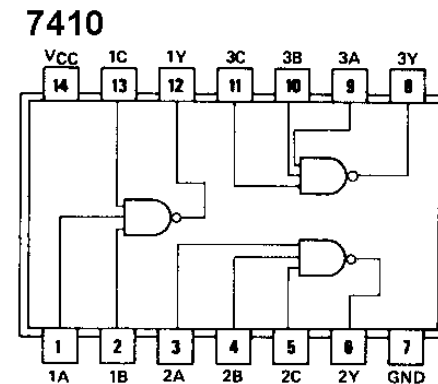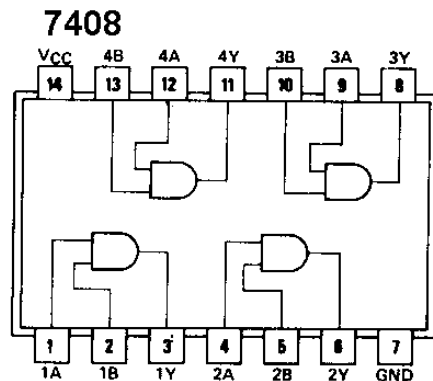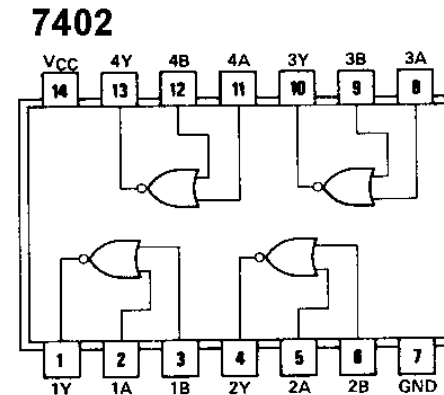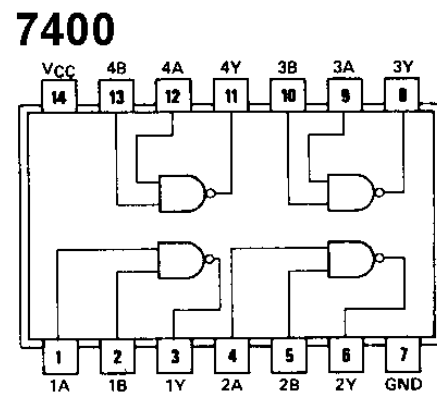
# Logic families

- 7400 series
  - Very popular as SSI and MSI devices in education
  - Initially a TTL family, there exist various compatible logic families in various technologies.



# Electrical parameters

---

- Supply voltage ( $V_{CC}$ )
- Logic levels
  - High and low
  - Input and output
  - Allow noise margin calculations
- Maximum current
  - Input ( $I_{IL}$ ,  $I_{IH}$ ). Lower is better.
  - Output ( $I_{OL}$ ,  $I_{OH}$ ). Higher is better.
  - Allow *fan-out* calculations.
- Power consumption
  - Static: when signals do not change.
  - Dynamic: when signals change.

# Electrical parameters

## recommended operating conditions

		SN54AS04			SN74AS04			UNIT
		MIN	NOM	MAX	MIN	NOM	MAX	
$V_{CC}$	Supply voltage	4.5	5	5.5	4.5	5	5.5	V
$V_{IH}$	High-level input voltage	2			2			V
$V_{IL}$	Low-level input voltage	0.8			0.8			V
$I_{OH}$	High-level output current	-2			-2			mA
$I_{OL}$	Low-level output current	20			20			mA
$T_A$	Operating free-air temperature	-55		125	0		70	°C

## electrical characteristics over recommended operating free-air temperature range (unless otherwise noted)

PARAMETER	TEST CONDITIONS	SN54AS04			SN74AS04			UNIT
		MIN	TYP <sup>§</sup>	MAX	MIN	TYP <sup>§</sup>	MAX	
$V_{IK}$	$V_{CC} = 4.5\text{ V}$ , $I_I = -18\text{ mA}$	-1.2			-1.2			V
$V_{OH}$	$V_{CC} = 4.5\text{ V to } 5.5\text{ V}$ , $I_{OH} = -2\text{ mA}$	$V_{CC} - 2$			$V_{CC} - 2$			V
$V_{OL}$	$V_{CC} = 4.5\text{ V}$ , $I_{OL} = 20\text{ mA}$	0.35	0.5		0.35	0.5	V	
$I_I$	$V_{CC} = 5.5\text{ V}$ , $V_I = 7\text{ V}$	0.1			0.1			mA
$I_{IH}$	$V_{CC} = 5.5\text{ V}$ , $V_I = 2.7\text{ V}$	20			20			μA
$I_{IL}$	$V_{CC} = 5.5\text{ V}$ , $V_I = 0.4\text{ V}$	-0.5			-0.5			mA
$I_{OII}$	$V_{CC} = 5.5\text{ V}$ , $V_O = 2.25\text{ V}$	-30		-112	-30		-112	mA
$I_{CCH}$	$V_{CC} = 5.5\text{ V}$ , $V_I = 0$	3	4.8		3	4.8	mA	
$I_{CCL}$	$V_{CC} = 5.5\text{ V}$ , $V_I = 4.5\text{ V}$	14	26.3		14	26.3	mA	

<sup>§</sup> All typical values are at  $V_{CC} = 5\text{ V}$ ,  $T_A = 25^\circ\text{C}$ .

<sup>¶</sup> The output conditions have been chosen to produce a current that closely approximates one half of the true short-circuit output current,  $I_{OS}$ .

# Electrical parameters

recommended operating conditions (see Note 4)

		SN54LS00			SN74LS00			UNIT
		MIN	NOM	MAX	MIN	NOM	MAX	
$V_{CC}$	Supply voltage	4.5	5	5.5	4.75	5	5.25	V
$V_{IH}$	High-level input voltage	2			2			V
$V_{IL}$	Low-level input voltage				0.7			V
$I_{OH}$	High-level output current				-0.4			mA
$I_{OL}$	Low-level output current				4			mA
$T_A$	Operating free-air temperature	-55			125			°C

NOTE 4: All unused inputs of the device must be held at  $V_{CC}$  or GND to ensure proper device operation. Refer to the TI application report, *Implications of Slow or Floating CMOS Inputs*, literature number SCBA004.

electrical characteristics over recommended operating free-air temperature range (unless otherwise noted)

PARAMETER	TEST CONDITIONST		SN54LS00			SN74LS00			UNIT
			MIN	TYP‡	MAX	MIN	TYP‡	MAX	
$V_{IK}$	$V_{CC} = \text{MIN}$ ,	$I_I = -18 \text{ mA}$				-1.5			V
$V_{OH}$	$V_{CC} = \text{MIN}$ ,	$V_{IL} = \text{MAX}$ ,	$I_{OH} = -0.4 \text{ mA}$						V
$V_{OL}$	$V_{CC} = \text{MIN}$ ,	$V_{IH} = 2 \text{ V}$	$I_{OL} = 4 \text{ mA}$		$I_{OL} = 8 \text{ mA}$				V
$I_I$	$V_{CC} = \text{MAX}$ ,	$V_I = 7 \text{ V}$				0.1			mA
$I_{IH}$	$V_{CC} = \text{MAX}$ ,	$V_I = 2.7 \text{ V}$				20			$\mu\text{A}$
$I_{IL}$	$V_{CC} = \text{MAX}$ ,	$V_I = 0.4 \text{ V}$				-0.4			mA
$I_{OS}§$	$V_{CC} = \text{MAX}$		-20		-100		-20		mA
$I_{CCH}$	$V_{CC} = \text{MAX}$ ,	$V_I = 0 \text{ V}$	0.8		1.6		0.8		mA
$I_{CCL}$	$V_{CC} = \text{MAX}$ ,	$V_I = 4.5 \text{ V}$	2.4		4.4		2.4		mA





† For conditions shown as MIN or MAX, use the appropriate value specified under recommended operating conditions.

‡ All typical values are at  $V_{CC} = 5 \text{ V}$ ,  $T_A = 25^\circ\text{C}$ .

§ Not more than one output should be shorted at a time.

# Electrical parameters


## Logic levels and noise margins

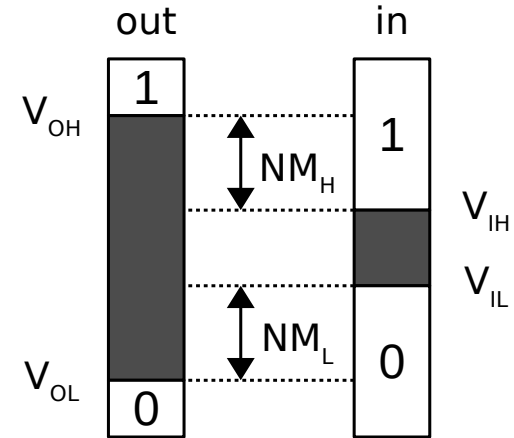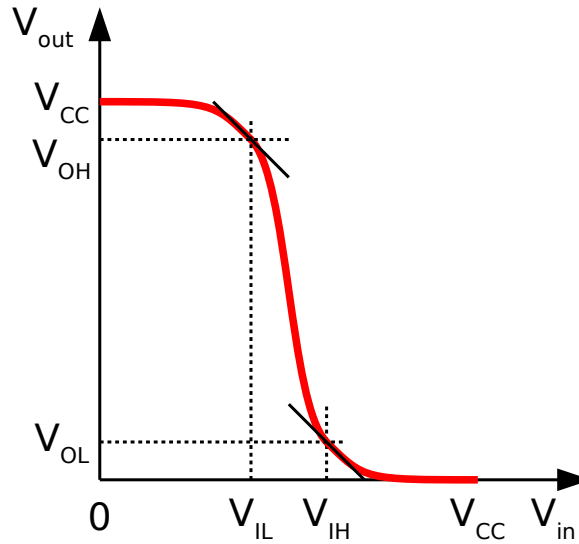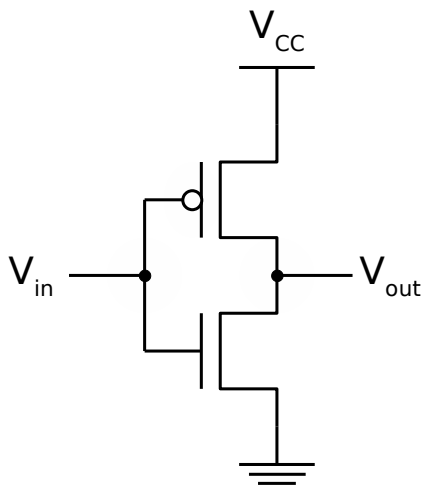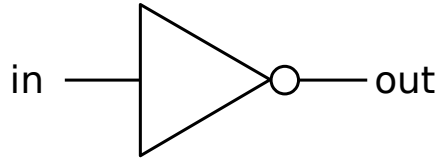

$$NM_L = V_{IL} - V_{OL}$$

$$NM_H = V_{OH} - V_{IH}$$


$$NM = \min(NM_L, NM_H)$$

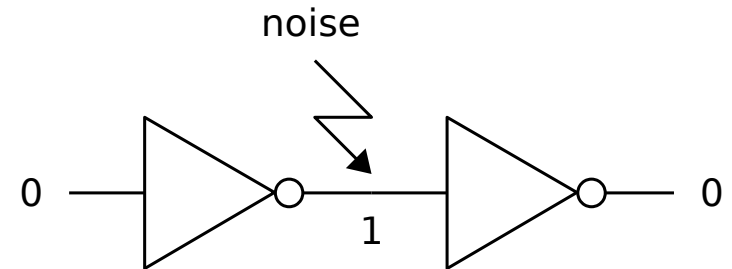

Simulation

# Electrical parameters

## Fan-out

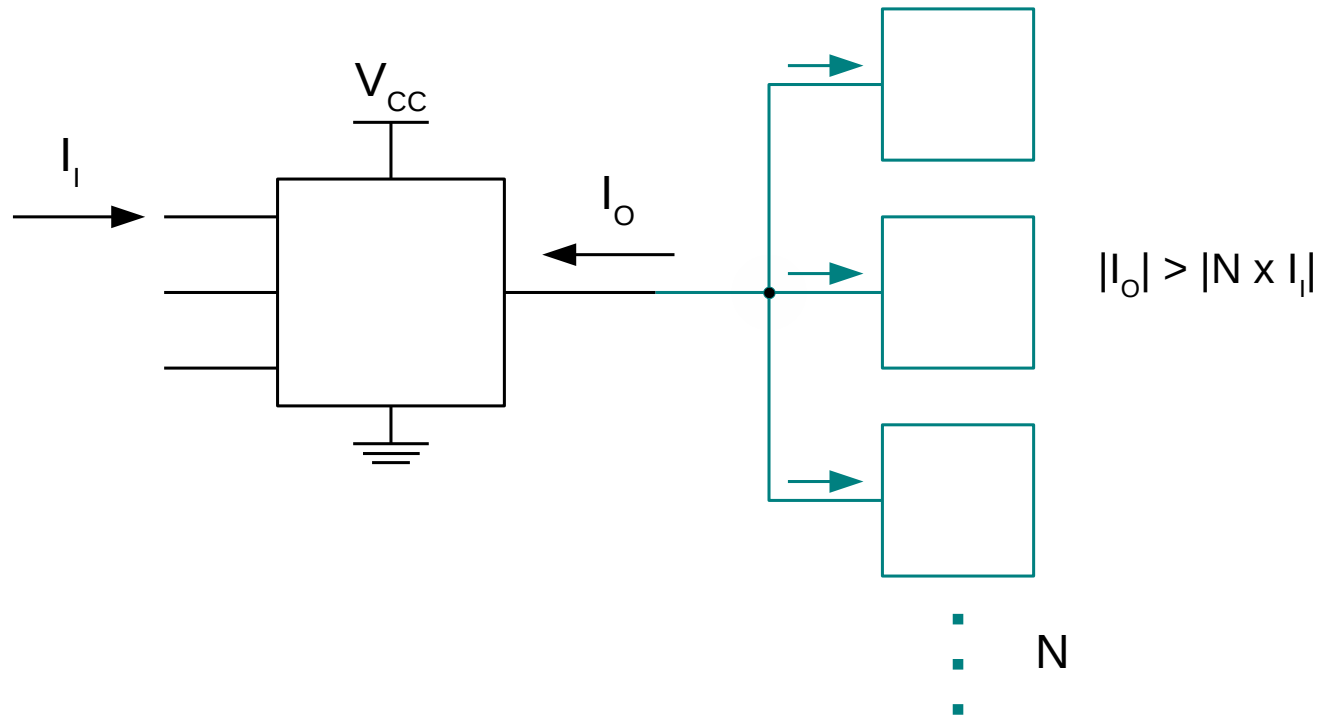

### FAN-OUT

Maximum value of N so that  $|I_o| > |N \times I_i|$  in both cases (high and low output levels)



# Electrical parameters

## Power consumption

---

- Static
- Dynamic
  - Depends on the frequency

$$P = VI$$

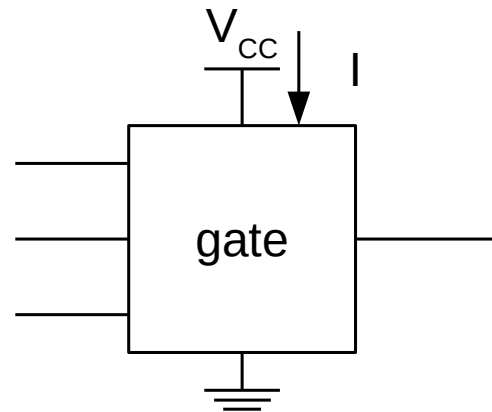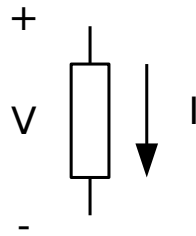

$$P = V_{CC} I$$





# Switching parameters

- Transition time: time for a transition to change from:
  - 10%  $V_{CC}$  to 90%  $V_{CC}$  (rising transition):  $t_{LH}$
  - 90%  $V_{CC}$  to 10%  $V_{CC}$  (falling transition):  $t_{HL}$
  - Depends on many factors, specially gate's strength and load.
- Propagation delay: time elapsed from the input transition to the output transition.
  - Two types: low-to-high ( $t_{pLH}$ ) and high-to-low ( $t_{pHL}$ ).
  - 50%  $V_{CC}$  as the reference for transitions.
  - Depends on many factors: gate design, output load (linear), etc.

switching characteristics,  $V_{CC} = 5\text{ V}$ ,  $T_A = 25^\circ\text{C}$  (see Figure 1)

PARAMETER	FROM (INPUT)	TO (OUTPUT)	TEST CONDITIONS	SN54LS00 SN74LS00			UNIT
				MIN	TYP	MAX	
$t_{PLH}$	A or B	Y	$R_L = 2\text{ k}\Omega$ , $C_L = 15\text{ pF}$		9	15	ns
$t_{PHL}$					10	15	

# Switching parameters

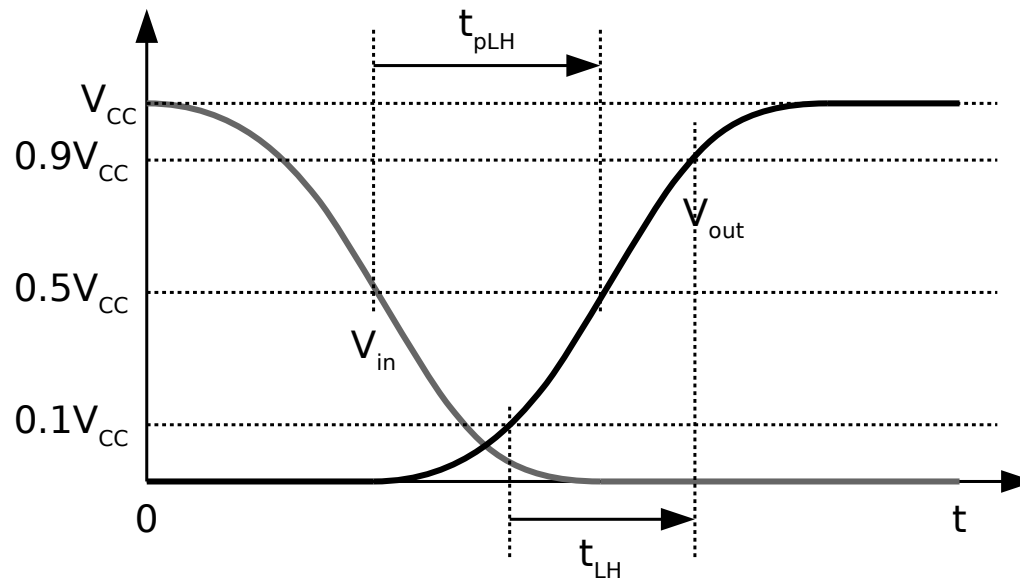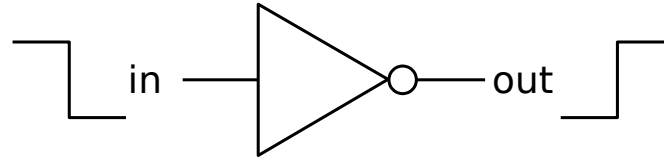

Simulation

Larger propagation delays make digital systems (computers) to run slower (smaller clock frequency)